
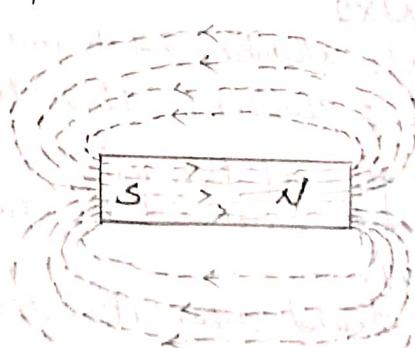


MAGNETIC CIRCUIT & COUPLE CIRCUIT

Magnetic circuit :-

Introduction :-

- Magnets are found in the natural state in the form of material called magnetic.
- Now a days natural magnets have no practical value. Because their magnetism is not strong enough to be utilise in the modern device.
- Magnetism is the force exerted (present/show) by magnets when they attract or repel each other.
- A magnet have two pole i.e., North pole and South pole.
- By convention the magnetic lines of force flow on the outside any magnet from North pole to South pole and inside of a magnet the field lines flow from South to North.
- Like pole repels each other & unlike pole attract each other.
- Magnetic field lines exist (show) around a magnet.
- The region (area) near the magnet where force of action of magnetic pole is called magnetic pole.
- The magnetic field is strongest near the pole and goes on decreasing in strength as we move away from the magnet.
- Magnetic field around a magnet is represented by imaginary lines is called magnetic lines of force or magnetic field lines & they never crush each other.

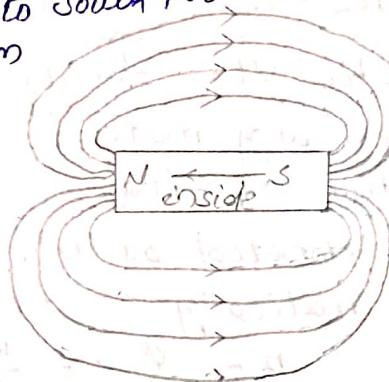

Magnetic Ckt! -

The representation of the system containing magnetic field, as an electrical network is called as Magnetic Circuit.

Magnetic Flux:-

The amount of magnetic field produced by a magnetic source is called as magnetic flux.

Quantitative:-

It is denoted by ϕ or field lines

SI unit of flux is Weber (wb)

1 weber = 10⁸ lines

The close path followed by magnetic flux is called magnetic circuit.

Magnetic Flux density:-

Magnetic flux density is the flux passing for unit area through any material through a right angle to a direction of flux.

It is denoted as 'B'.

Mathematically

$$B = \frac{\phi}{\text{area}} = \frac{\text{Weber}}{\text{m}^2}$$

SI unit of magnetic flux density (B) = $\frac{\text{WB}}{\text{m}^2}$

Magnetic force (mmf) :-

It required to derived the magnetic flux in the magnetic circuit.

The SI unit of mmf is Amper turn.

$N \times I$

I = current flow through the magnetic ch.

The strength of the mmf is equivalent to the product of the current around the turns and the number of turns of the coil.

Magnetic field Intensity/ magnetic force (H) :-

It is magnetic force per unit area.

It is denoted by 'H'.

So mathematically $H = \frac{\text{mmf}}{l} = \frac{\text{Amper turn per meter}}{\text{meter}} = \text{A.T per meter}$

SI unit of magnetice field Intensity is AT/m

Note:-

$$\delta = \frac{\text{mmf}}{\text{Reluctance}} = \frac{\text{AT}}{\text{Air volume}}$$
$$= \frac{\delta}{a} \times \frac{1}{\mu_0 \mu_r}$$
$$= B \times \frac{1}{\mu_0 \mu_r}$$
$$\therefore AT = \frac{B}{\mu_0 \mu_r} \times l$$

Relation between 'B' & 'H' :-

$$B \propto H$$

$$B = \epsilon_1 H \quad (\epsilon_1 = \text{constant})$$

$$\epsilon_1 = \frac{B}{H} \quad \therefore H = \epsilon_0 - \epsilon_1$$

$$\text{also } [B = \epsilon_1 \epsilon_0 H]$$

Where, ϵ_1 = absolute permittivity of the material

ϵ_0 = relative permittivity of the material

ϵ_0 = absolute permittivity of air & vacuum

On air or vacuum, the relative permittivity is 1 so

$$\epsilon_1 = \epsilon_0$$

Permeability:-

Permeability of a material means its conductivity for magnetic flux.

Greater the permeability of a material, the greater is its conductivity for magnetic flux and vice-versa.

Conductivity of magnetic conductor of magnetic

air or vacuum is the poorest conductor of magnetic flux.

It is denoted by μ .

The absolute permeability (μ_0) of air or vacuum (back or standard medium) is $4 \times 10^{-7} \text{ H/m}$ or (Henry/meter). But the absolute permeability of magnetic material is much greater than 10^6 .

→ The ratio of μ_{air} is called the relative permeability of the material and is denoted by μ_r .

$$\mu_r = \frac{\mu}{\mu_{air}}$$

→ μ_r for air or vacuum would be $\frac{\mu_0}{\mu_{air}}$ = 1

→ Extra state :-

→ The value of μ_r for all non-magnetic material is also 1.

→ The value μ_r for magnetic material is very high.

Ex:- Iron = 8000 (pure iron)

Reluctance :-

→ The opposition offered to magnetic flux by magnetic circuit is called reluctance.

→ The reluctance in a magnetic ckt depends upon its length, area of cross-section and permeability of the material that make up the magnetic ckt.

→ SI's unit is A^2/Wb

$$S = \frac{mm^2}{A} = \frac{A^2}{\mu} = \frac{1}{\mu_r} = \text{atm/Am}$$

Permeance :- (It is reciprocal of conductance)

→ It is reciprocal of reluctance which can passes flux through the material.

SI unit is At/m

$$\text{Permeance} = \frac{A}{\text{reluctance}} = \frac{A^2}{\mu_r} = \frac{A^2}{\mu}$$

* Difference between electric field & magnetic field

Electric field


Magnetic field

→ Flow of current is the cause of flow of magnet is the cause of flow of flux.


→ Opposition offered to the flow of current is the cause of opposition offered to the flow of flux.

→ Conductance = $\frac{1}{Resistance}$

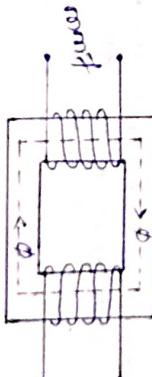→ $\frac{1}{Resistance} = \frac{Current}{Voltage}$



→ Core type

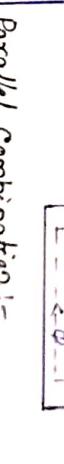

→ Shell type

Parallel Combination :-
In magnetic ckt if flux gets divided into two or more than two paths then it is said to be parallel combination.

$$\frac{1}{S} = \frac{1}{S_1} + \frac{1}{S_2} + \frac{1}{S_3} + \dots + \frac{1}{S_n}$$

$$\rightarrow shell type$$

B-H curve / Hysteresis curve :-

The saturation of magnetic circuit can be easily obtained by the use of B-H curve.

Magnetic field
Magnetic field
→ Flux doesn't actually flow in an
magnetic ckt.

→ Energy is initially needed to create
the magnetic flux but not to
maintain it.

→ Conductance is constant and
independent of current temp.
Strength at a particular temp.

→ Energy is initially needed to create
the magnetic flux but not to
maintain it.

Series & Parallel magnetic circuit :-

Series Combination :-

On series combination of a magnetic ckt the magnetic flux through different parts of magnetic ckt should be same.

$$S = S_1 + S_2 + S_3 + \dots + S_n$$

(S = reluctance)

Series Combination of magnetic circuit :-


is corresponding to the flux density (B) in the material along the

magnetising force ' H ' from B-H curve of the material.

In compute the magnetic length ' l '.

We can use formula but we don't use B-H curve to find out. We can use μ_0 and μ_r but we don't use B-H curve to find out.

Hysteresis loop:-

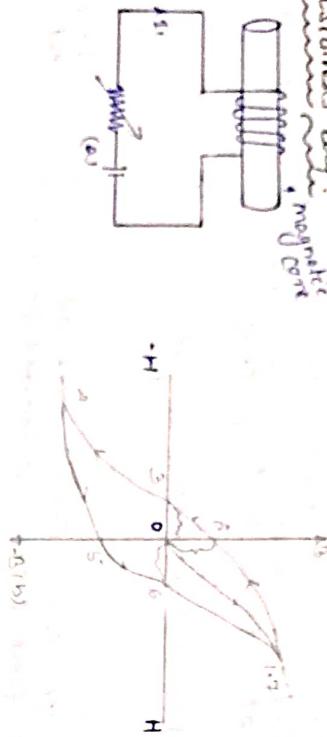

From figure when $B = 0$ i.e. $H = \frac{M}{\mu_0} = 0$ and $B = 0$, this is represented by point '0' in the graph.

\Rightarrow The current in the coil increased ' H ' increases and so does ' B '. The 'B-H' curve follows the path 0-1 and point '1' is the beginning of magnetic saturation. Here all of the domains in the core material have become perfectly aligned.

\Rightarrow Now ' H ' is reduced by decreasing current in the wedge the curve follow the path 1-2. Note that after magnetic saturation has been reached (Point 1), then decreasing ' H ' does not reduce ' B ' along the same curve that it followed when it was increased.

At point '2'; $H = 0$, but ' B ' has finite value, this lagging of ' B ' behind ' H ' is called hysteresis. Actually the fact is the magnetic domain retain their alignment to some extent after the magnetising force is reduced or removed. So thus flux density is said to be residual flux density (0-2), it remains in the core after the current is reduced to zero.

The degree to which magnetic material retains its magnetism after the magnetising force is reduced to zero is called

Retentivity.

\Rightarrow If direction of ' H ' is reversed by reversing the current, and the B-H curve followed the path 2-3. Then a considerable amount of ' H ' is required to reduce the flux density to zero. The -ve value of ' H ' required to reduce residual flux density to zero is called coercive force.

Q: If ' H ' is now reduced, ' B ' decreases and follows the path 4-5. Note that point '5' is the residual flux density and same as to point 0.

If the direction of ' H ' is now reverse so that is again pointing to zero. Note that ' B ' remains -ve until it is made sufficiently +ve to bring ' B ' back zero (Point 6). Further increase of ' H ' causes ' B ' to increase towards +ve saturation at point 1.

The Compute B-H curve 1-2-3-4-5-6-1 is called the hysteresis loop.

CURRENT CIRCUIT

- When the magnetic flux linking a conductor or coil changes, an emf is induced in that conductor.
- If coil produced a "flux 'Φ'" and the coil has 'n' no. of turns then the flux linking is

$$\Psi = N\Phi$$

$$\text{or, } e = N \frac{d\Phi}{dt}$$

$$e = -N \frac{d\Phi}{dt} \text{ (According to Lenz's law)}$$

Flux linkage :-

Total flux passing through a coil of 'N' turns.

⇒ The changes in flux linkage can be brought about in the following two ways.

1) Dynamically induced emf
2) Statistically induced emf

1) Dynamically induced emf :-

The conductor is moved into the stationary field in such a way that the flux linking it, changes in magnitude. The emf induced in this way is called "dynamically induced emf".

→ In short form → Emf is produced in the conductor which is statitically induced emf :-

2) Statistically induced emf :-

The conductor is stationary and the magnetic field is moving or changing. The emf induced in this way is called statically induced emf.

→ A statically induced emf can be further sub divided into

A) Self induced emf
B) Mutually induced emf

A) Self induced emf :-

The emf induced in a coil due to the change of its own flux linked with it is called self induced emf.

→ When current in a coil increases or decreases, there is a change in magnetic flux linking in the coil. Hence an emf induced in the coil. The process is called self-induced emf.

$$e = N \frac{d\Phi}{dt}$$

According to Lenz's law, the direction of this induced emf is such that it opposes the cause that has produced it. Now the cause of this induced emf is the change in magnetic flux through the coil i.e. change of current in the coil. Hence the induced emf will oppose the change of current in the coil. This property of the coil is called its self-inductance or inductance (L).

$$e = -N \frac{d\Phi}{dt}$$

Self Inductance (L) :-

→ The property of a coil by virtue of which it opposes any change in the amount of current flowing through it, is called it's self inductance or inductance (L).

$$\Rightarrow e = -N \frac{d\Phi}{dt}$$

$$\Rightarrow e = -\frac{d}{dt}(N\Phi)$$


⇒ $N\Phi = I$ (As per law of conservation of energy)

⇒ $\frac{d}{dt}(N\Phi) = \frac{d}{dt}(NI)$ (As per law of conservation of energy)

⇒ $N\frac{d\Phi}{dt} = NI$ (∴ L = proportionality constant)

→ It's unit is Henry.

$$L = \frac{\Psi}{I} = \frac{N\Phi}{I}$$

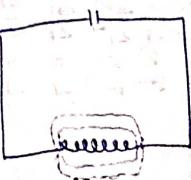

Inductance of solenoidal coil (or coil):

$$\Psi = LI$$


$$I = \frac{N\phi}{L} = \frac{\Psi}{L}$$

$$L = \frac{N\phi}{I}$$

$$L = N \frac{d\phi}{dt}$$

Actually, $\phi = \frac{mmf}{\text{reluctance}} = \frac{NI}{\text{reluctance}}$
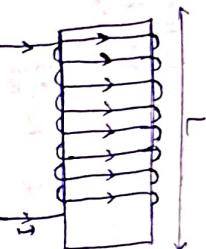
$$\frac{d\phi}{dt} = \frac{N \text{a} \text{mper}}{l}$$



Area of cross section.

Differentiating ϕ w.r.t. t , we get

$$\frac{d\phi}{dt} = \frac{N \text{a} \text{mper}}{l} = \frac{L}{N} = \frac{Na \text{mper}}{l}$$

$$= L = N^2 a \text{ mhos}$$

$$\Rightarrow L = \frac{N^2}{l} a = \frac{\text{Reluctance}}{N^2}$$

Induced emf is directly proportional to turns swept and inversely proportional to the reluctance of the magnetic path.


An iron-coated coil has more inductance than the equivalent air coated coil.

A coil is said to have large self inductance if it produces a large induced emf.


The value of "L" depends upon the dimensions of the coil, no. of turns and the relative permeability of the core material.

Mutually Induced emf = $\frac{\Delta \Psi}{\Delta t} = \frac{\Psi_2 - \Psi_1}{\Delta t}$

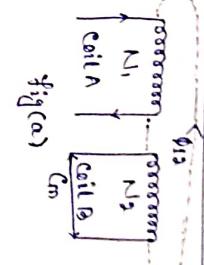The induced emf in a coil due to the changing current in the neighbouring coil is called mutually induced emf (emf).



Fig(a)

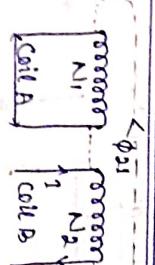

Fig(b)

Consider the above two coils, A & B placed near each other. Coil "B" is not electrically connected coil "A".

If current "I₁" flowing through coil "A", the magnetic field is set up and the part of $C(\phi_1)$ this flux links with coil "B", its current in coil "A" is changed, the mutual flux also changes and hence an emf is induced in coil "B". The emf induced in coil "B" is named as mutual induced emf. and the process is known as mutual induction.

According to Faraday's Law of electromagnetic induction

$$\text{emf} = -N_2 \frac{d\phi_2}{dt}$$

Similarly

$$\text{emf} = -N_1 \frac{d\phi_1}{dt}$$

Mutual Inductance (M) :-

The property of two coils by virtue of which each opposes any change of current flowing in the other is called mutual inductance bet' two coil.

This opposition occurs because a changing current in one coil produces mutually induced emf in the other coil which opposes the changing of current in the first coil.

$$N_1 \phi_{12} \propto I_1$$

$$\text{emf}_1 \propto -\frac{d\phi_{12}}{dt} = \frac{d\phi_{12}}{dt} = M \frac{dI_1}{dt}$$

$$\text{emf}_2 \propto -\frac{d\phi_{21}}{dt}$$

$$\text{emf}_2 = -M \frac{dI_2}{dt}$$

Mutual Inductance (M) :-

$$\rightarrow M = \frac{\phi_{12}}{I_2}$$



$$\boxed{\phi_{12} = \phi_u + \phi_{12}}$$

$\phi_{12} \rightarrow$ Mutual flux from coil 1 to coil 2.

$$\begin{aligned} \text{Given } I_1 &= \text{current in primary coil} \\ \text{Given } \phi_u &= \text{flux due to primary current} \\ \text{Given } \phi_{12} &= -m \frac{d\phi_1}{dt} \end{aligned}$$

$$\begin{aligned} \text{Given } I_2 &= \text{current in secondary coil} \\ \text{Given } \phi_{12} &= -N_2 \frac{d\phi_{12}}{dt} \end{aligned}$$


$$\text{neglecting } \phi_u \rightarrow m \frac{d\phi_1}{dt} = -N_2 \frac{d\phi_{12}}{dt}$$

$$\begin{aligned} \rightarrow \frac{d\phi_1}{dt} (N_{12}) &= N_2 \frac{d\phi_{12}}{dt} \\ \rightarrow M_{12} &= N_2 \phi_{12} \end{aligned}$$

$$\boxed{M = \frac{N_2 \phi_{12}}{T_1}}$$

Mutual Inductance depends on mutual flux.

Similarly if from current I_2

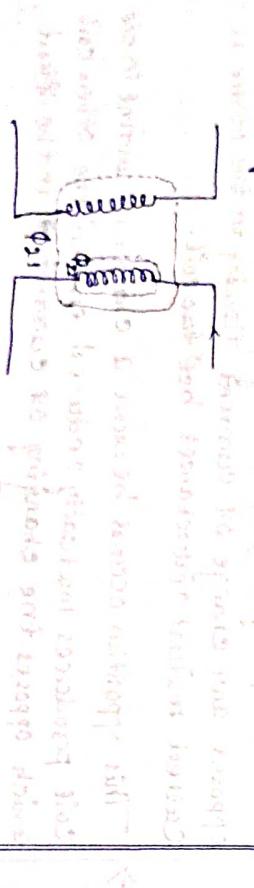

$$\boxed{\phi_{21} = \phi_u + \phi_{21}}$$

$$\boxed{M = \frac{N_1 \phi_{21}}{T_2}}$$

$$\boxed{M = \frac{N_1 \phi_{21}}{T_2} = \frac{N_1 \phi_{21}}{Amp}}$$

It is called **Hensity**.

Coefficient of coupling (K) :-

It represents the flux linking capacity of coil.

Or

The fraction of total flux links the other coil is represented by coefficient of coupling.

$$K = \frac{\phi_{12}}{\phi_2} = \frac{\text{Mutual Flux}}{\text{Total Flux}}$$

$$\begin{aligned} K &= \frac{\phi_{12}}{\phi_2} = \frac{\text{Mutual Flux}}{\text{Total Flux}} \\ &\text{or } \phi_{12} = K \phi_2 \end{aligned}$$

The value of "K" varies with 0 to 1.

i) if $K=0$ then Mutual flux = 0

or ϕ_{12} or $\phi_{21} = 0$

These values of it is loosely coupled or isolated couple.

ii) if $K=1$ then Maximum mutual flux.

it is tightly coupled circuit.

$M = N_1 \phi_{21}$ (for coil 1) $\sim \sim \sim$ ①

$$M = \frac{N_2 \phi_{12}}{T_1} (\text{from coil 2}) \sim \sim \sim$$
 ②

Multiply eqn ① & ②

$$\rightarrow m^2 = \frac{N_1 \phi_{21}}{T_2} \times \frac{N_2 \phi_{12}}{T_1} \times \frac{\phi_{12}}{\phi_2}$$

$$\rightarrow m^2 = \frac{N_1 \phi_{21}}{T_1} \times \frac{N_2 \phi_{12}}{T_2} \times \frac{\phi_{12}}{\phi_1} \times \frac{\phi_{12}}{\phi_2}$$

$$\therefore m^2 = L_1 \times L_2 \times K^2$$

$$m^2 = L_1 L_2 K^2$$

$$\boxed{m = K \sqrt{L_1 L_2}}$$

$$\boxed{k = \frac{M}{\sqrt{L_1 L_2}}}$$

$$0 < k < 1$$

$$\Rightarrow 0 < \frac{M}{\sqrt{L_1 L_2}} < 1$$

$$\Rightarrow 0 < M < \sqrt{L_1 L_2}$$

for maximum mutual inductance

$$\boxed{M = \sqrt{L_1 L_2}}$$

Dot Convention :-

Dot Convention is technique, which gives the direction of voltage polarity at the dotted terminal.

If the current enters at the dotted terminal of core (Inductor) then it induces a voltage at another coil (Inductor) which is having -ve polarity at the dotted terminal.

If the current leaves from dotted terminal of one coil (Inductor) then it induces a voltage at another coil (Inductor) which is having +ve polarity at the dotted terminal.

Classification of coupling :-

We can classify coupling into the following categories.

1. Electrical coupling
2. Magnetic coupling

Electrical coupling :-

Electrical coupling occurs, when there exist a physical connection between two coils (inductors).


This coupling can be either of aiding type or opposing polarity type.

The electrical connection of two coil is either series type or parallel type.

We have discussed two connection.

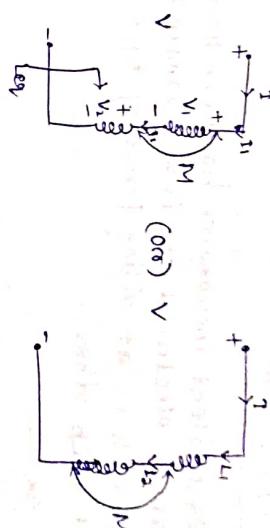1. Series type (aiding & opposing)
2. Parallel type (aiding & opposing)

Coupling of coupling polarity type:-
In electric circuit, which is having two inductors that are connected in series.



from figure

$$I_1 = I_2 = I \quad \dots \dots \dots \textcircled{i}$$

$$V_1 = L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt}$$

$$V_2 = L_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt}$$

$$V = V_1 + V_2 \dots \dots \dots \textcircled{ii}$$

$$\Rightarrow V = L_1 \frac{dI_1}{dt} + M \frac{dI_2}{dt} + L_2 \frac{dI_2}{dt} + M \frac{dI_1}{dt}$$

$$\Rightarrow V = (L_1 + L_2 + 2M) \frac{dI}{dt} \dots \dots \textcircled{iii}$$


$$\Rightarrow V = L_{eq} \frac{dI}{dt} \text{ where } \textcircled{iv}$$

Comparing eqn \textcircled{iii} & \textcircled{iv}

$$\boxed{L_{eq} = L_1 + L_2 + 2M}$$

Opposing Polarity type :-

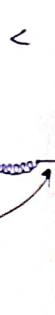Similarly, one is dot to coil and another is coil to dot. Then and coil to dot and dot to coil (in fig(2)). Then



$$L_{eq} = L_1 + L_2 - 2m$$


→ The equivalent inductance of series combination of inductor is

$$L_{eq} = L_1 + L_2 \pm 2m$$

→ In this case, the equivalent inductance has been increased by $2m$. Hence the above electrical circuit is an example of electrical coupling which is at aiding property type (their fluxes aids each other).

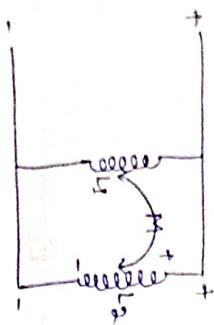2) Referred equivalent circuit :-

→ when the two inductors are connected in parallel.



→ The total or effective inductance L_{eq} of two coils is given by.

i) Fluxes adding

$$L_{eq} = \frac{L_1 L_2 - m^2}{L_1 + L_2 - 2m}$$

ii) Fluxes opposing

$$L_{eq} = \frac{L_1 L_2 - m^2}{L_1 + L_2 + 2m}$$

→ if there is no mutual inductance bet' two coils ($m=0$) then,


$$L_{eq} = \frac{L_1 L_2}{L_1 + L_2 + 2m}$$

$$L_{eq} = \frac{L_1 + L_2}{L_1 + L_2}$$

$$L_{eq} = \frac{L_1 L_2 - m^2}{L_1 + L_2 - 2m}$$

$$L_{eq} = \frac{L_1 L_2 - m^2}{L_1 + L_2 + 2m}$$
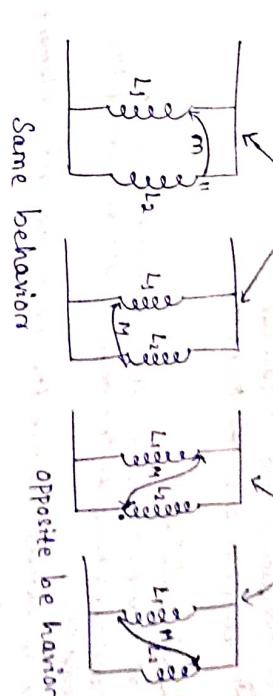
$$L_{eq} = \frac{L_1 L_2 - m^2}{L_1 + L_2}$$



Same behavior

opposite behavior

Circuit element and analysis

- circuit is a network providing one or more closed path, where a network is an interconnection of element or devices.
- Circuit Analysis is the process of determine voltage across component through the element of the ckt.
- The network or ckt element may be classified as 9 groups:-

 - ① Active and passive
 - ② Linear and Non-linear
 - ③ Unilateral and Bilateral
 - ④ Lumped and distributed

Active & Passive Element:-


- On case of $v-t$ plane, char. of passive element offers only positive impedance. Where as the char. of active element offers negative impedance.
- Normally, passive element absorb the energy and active element devoring the energy.
- Active element control the flow of energy where as passive element dissipated or stored the energy.

Example of Active Elements:-


- (i) voltage source
- (ii) Current source
- (iii) Generator

Example of Passive Elements:-

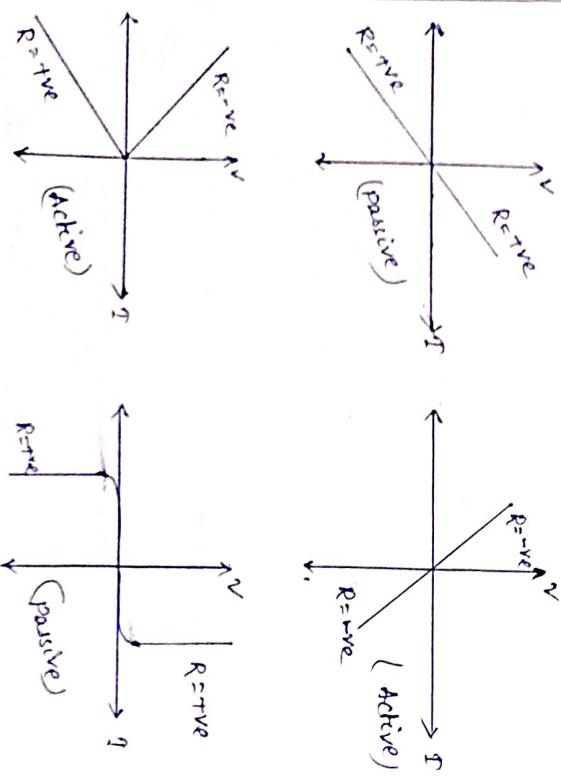- (i) Capacitor
- (ii) Inductor
- (iii) Resistor



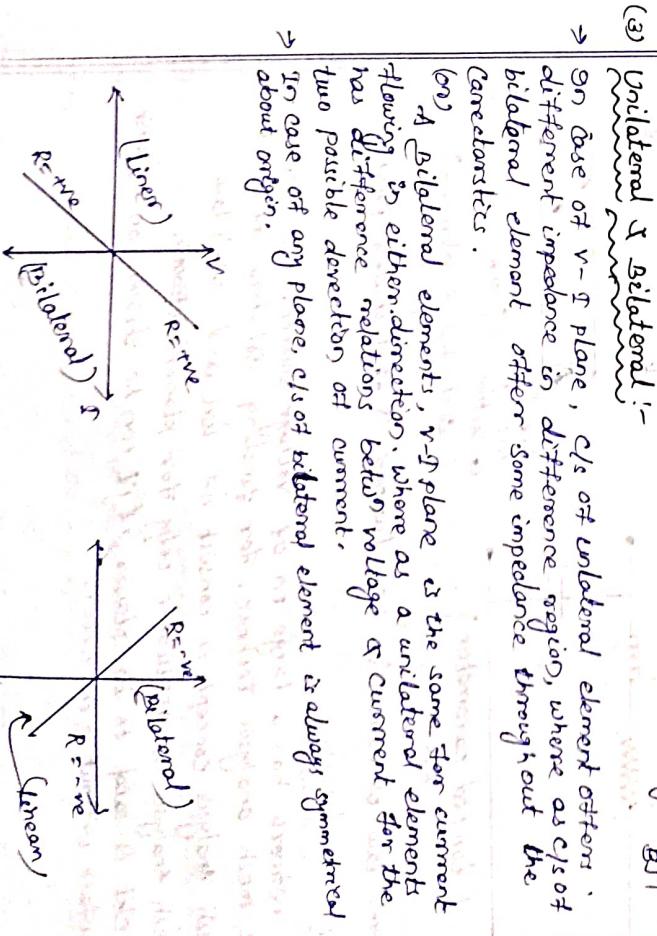
1st & 3rd quadrant → Passive
2nd & 4th quadrant → Active




Unilateral & Bilateral:-

- On case of $v-t$ plane, ckt is unilateral element offers different impedance in difference regions, where as ckt of bilateral element offers same impedance throughout the connections.

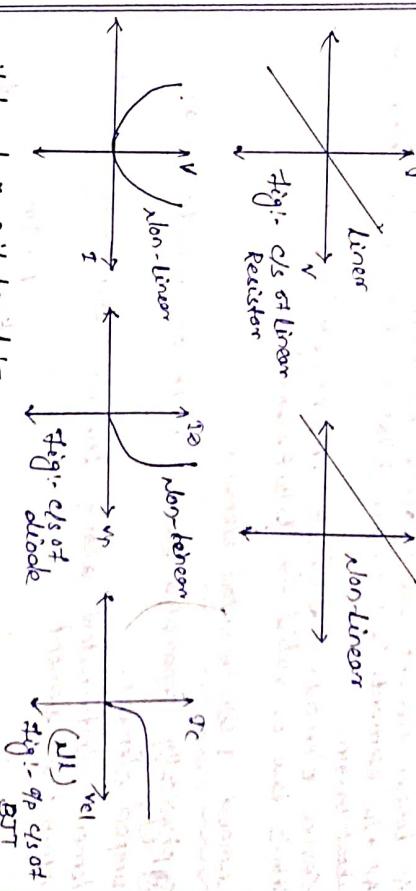- A bilateral element's $v-t$ plane is the same for current flowing in either direction, where as a unilateral element has different relations between voltage & current for the two possible direction of current.
- In case of any plane, ckt of bilateral element is always symmetrical about origin.



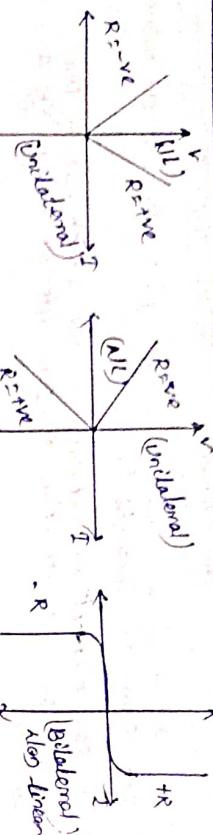- (2) **Linear & Non-Linear Element:-**
- The char. of linear element always passes through the origin in the form of straight line.
- A linear element or network is one which satisfies the principle of superposition i.e. principle of homogeneity & additivity.
- The element which doesn't satisfy the above principle is called Non-linear element.



\rightarrow Fig:- Symm about V -axis
 \rightarrow Symm about R -axis


\rightarrow All linear elements are bilateral but nonreciprocal not true.

\rightarrow All of low elements (R, L, C) are bilateral because it's el's is symm about origin.
 \rightarrow Device Elements (C Diode, BJT, MOSFET etc.) are unilateral.
 \rightarrow Ohm's law is valid for L, B , C element.

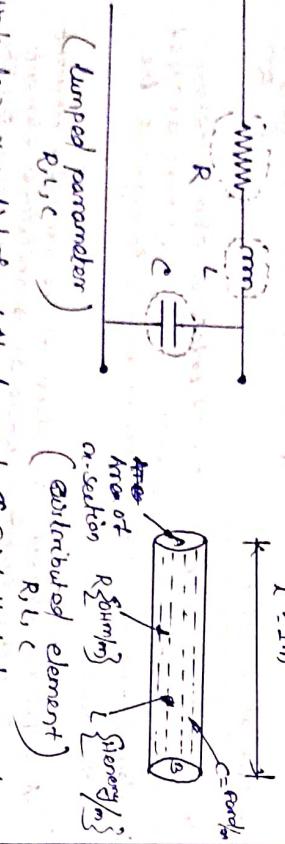(4) Lumped & Distributed element:-

\rightarrow physically separated element in the el's is referred as lumped element.

\rightarrow Element distributed along the line then it is referred as distributed element.



\rightarrow Ohm's law is valid for both lumped & distributed parameter.


Mesh analysis:-

- \rightarrow A network has a large no. of voltage sources, it is useful to use mesh analysis technique. For finding solution of a network, mesh analysis concept is consist of VCR and Ohm's law.
- \rightarrow mesh analysis is applicable only for planer network.
- \rightarrow A netw is said to be planer if it can be drawn on a plane surface without crossover.

Condition for mesh analysis:- (VCR + Ohm's law)

- \rightarrow Temperature is constant
- \rightarrow L, B, ρ
- \rightarrow lumped electrical el's

Example:-

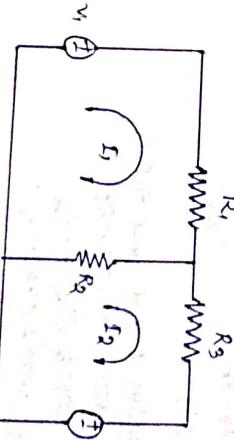

Applying VCR in mesh -1



$$\Rightarrow v_1 - I_1 R_1 - C(I_1 - I_2) R_2 = 0 \quad \dots \quad (1)$$

Applying VCR in mesh -2

$$\Rightarrow +R_2 (I_2 - I_1) - I_2 R_3 - v_2 = 0 \quad \dots \quad (2)$$


- \rightarrow The Branch current may be different or same from the mesh current.
- \rightarrow The no. of mesh currents is equal to the no. of mesh esp
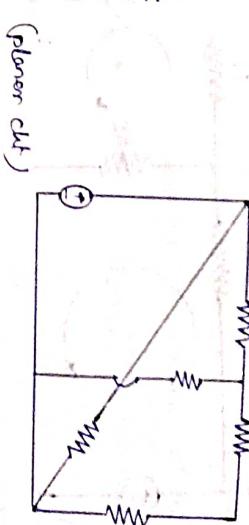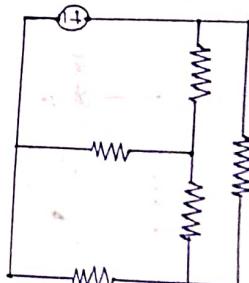
$$\rightarrow \text{No. of equations} = \text{Branches} - (\text{Nodes} - 1)$$



Mesh Equation By Inspection Method:

The loop equation are

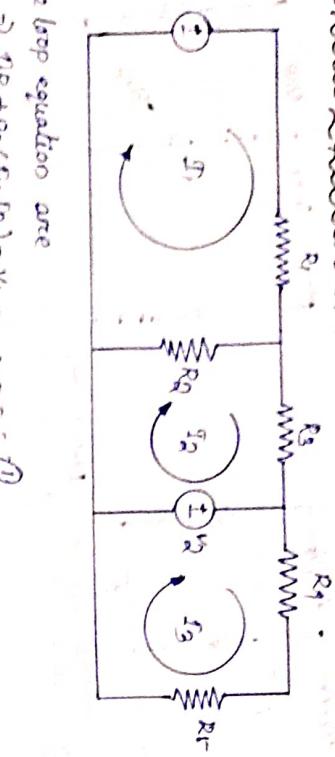

$$\begin{aligned} & \Rightarrow RI_1 + R_2(I_2 - I_1) = V_1 \quad \text{--- (1)} \\ & \Rightarrow R_2(I_2 - I_1) + R_3R_3 = -V_2 \quad \text{--- (2)} \\ & \Rightarrow R_3I_3 + R_2I_2 = V_2 \quad \text{--- (3)} \end{aligned}$$

Rearranging the above eqn

$$\begin{aligned} & \Rightarrow (R_1 + R_2)I_1 - R_2I_2 + V_1 = 0 \quad \text{--- (4)} \\ & \Rightarrow -R_2I_1 + (R_2 + R_3)I_2 = -V_2 \quad \text{--- (5)} \\ & \Rightarrow (R_2 + R_3)I_3 = V_2 \quad \text{--- (6)} \end{aligned}$$

The general mesh eqn for the three-mesh resistive network

$$R_1I_1 + R_2I_2 + R_3I_3 = V_a \quad \text{--- (7)}$$

$$R_2I_1 + R_3I_2 + R_1I_3 = V_b \quad \text{--- (8)}$$

$$R_3I_1 + R_1I_2 + R_2I_3 = V_c \quad \text{--- (9)}$$

By comparing the equation 7, 8, 9 and 4, 5, 6

$$\begin{aligned} & \text{Left resistance of loop-1 } (R_{11}) = R_1 + R_2 \\ & \text{mutual resistance of loop-2 } (R_{21}) = -R_2 \\ & \text{voltage which drives loop-1 } (V_a) = V_1 \end{aligned}$$

$$R_{11} = 0 \quad \text{--- (10)}$$

$$\begin{aligned} & \text{Left resistance of loop-2 } (R_{22}) = R_2 + R_3 \\ & \text{mutual resistance of loop-2 } (R_{12}) = R_2 \\ & \text{voltage which drives loop-2 } (V_b) = V_2 \end{aligned}$$

$$R_{22} = 3 + 4 = 7 \Omega \quad \text{--- (11)}$$

$$\begin{aligned} & \text{Left resistance of loop-3 } (R_{33}) = R_3 + R_1 \\ & \text{mutual resistance of loop-3 } (R_{23}) = -R_3 \\ & \text{voltage which drives loop-3 } (V_c) = V_3 \end{aligned}$$

$$R_{33} = 6 + 4 = 10 \Omega \quad \text{--- (12)}$$

$$R_{23} = 0 \quad \text{--- (13)}$$

$$\begin{aligned} & \text{Left resistance of loop-3 } (R_{33}) = R_3 + R_1 \\ & \text{mutual resistance of loop-3 } (R_{31}) = R_3 \\ & \text{voltage which drives loop-3 } (V_c) = V_3 \end{aligned}$$

$$R_{31} = 0 \quad \text{--- (14)}$$


$$R_{32} = 0 \quad \text{--- (15)}$$

$$V_C = V_3 \quad \text{--- (16)}$$

If current passing through the common resistance are the same, the mutual resistance will have a positive sign, and if the direction of the currents passing through the common resistance are opposite then the mutual resistance will have a negative sign.

\rightarrow Voltage of loop is positive sign used if the direction of the current is the same as the direction of the source. If the current direction is opposite to the direction of the source, then the -ve sign is used.

Example:-

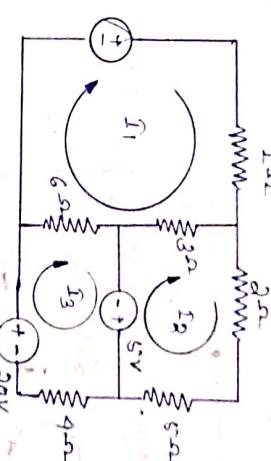

Solution:-

The general equation for 3-mesh network

$$R_1I_1 + R_2I_2 + R_3I_3 = V_a$$

$$+ R_2I_1 + R_3I_2 + R_1I_3 = V_b$$

$$+ R_3I_1 + R_1I_2 + R_2I_3 = V_c$$

Comparing the above figure,

$$R_{11} = 1 + 3 + 6 = 10$$

$$R_{12} = 3\Omega \quad \text{--- (17)}$$

$$R_{13} = 6\Omega$$

$$V_a = +10V$$

$$R_{21} = -3\Omega$$

$$R_{22} = 3 + 4 = 7\Omega \quad \text{--- (18)}$$

$$R_{23} = 0$$

$$V_b = -5V$$

$$R_{31} = 6\Omega$$

$$R_{32} = 0$$


$$V_c = -6V \quad \text{--- (19)}$$

$$R_{33} = 10\Omega \quad \text{--- (20)}$$

$$V_c = (R_{31} + R_{33})I_3 = 25V$$

Concept of Supermesh:-

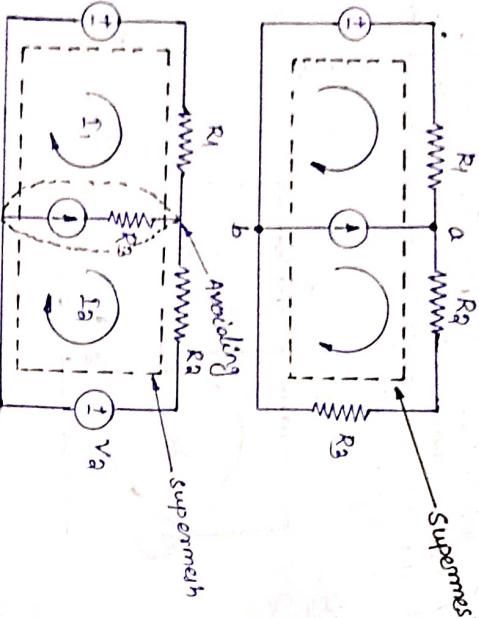If a current source (independent or dependent) is common between two mesh, we can treat a supermesh by avoiding the current source and only elements connected in series with it.



mesh Analysis = KVL + Ohm's law

Supermesh = KVL + Ohm's law + iuc

KCL (Sm) \Rightarrow Applied total cut:-

$$\Rightarrow -V_1 + I_1 R_1 + I_2 R_2 + V_2 = 0 \quad \dots \text{①}$$

KCL (Sm):

$$I = I_2 - I_1 \quad \dots \text{②}$$

$$I = I_1 - I_2 \quad \dots \text{③}$$

By using mesh Analysis:-

From mesh-1

$$\Rightarrow -V_1 + I_1 R_1 + V = 0 \quad \dots \text{④}$$

For mesh-2

$$\Rightarrow -V_2 + I_2 R_2 + V_2 = 0 \quad \dots \text{⑤}$$


Add the above two equations:-

$$\Rightarrow -V_1 + I_1 R_1 + I_2 R_2 + V_2 = 0 \quad \dots \text{⑥}$$

\hookrightarrow supermesh (uvleg)

$$KCL: \quad I_2 - I_1 = 2A \quad \dots \text{⑦}$$

Example 11:-

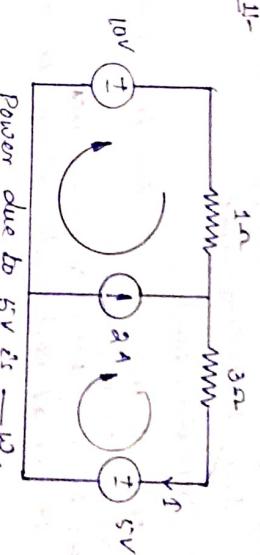

Gold

KVL (Sm)

$$\Rightarrow -10V + 1 \times I_1 + 3I_2 + 5V = 0$$

$$\Rightarrow I_1 + 3I_2 = 5 \quad \dots \text{①}$$

KCL (Sm)

$$\Rightarrow I_2 = I_1 - I_3 \quad \dots \text{②}$$

Adding eqn ① & ②

$$\Rightarrow 5 = 5 + 3I_2$$


$$\Rightarrow I_2 = I_1 + I_3$$

$$I_1 = 4I_2$$

$$\Rightarrow I_2 = \frac{5}{4} A = 1.25$$

$$P_{Gr} = 5 \times \frac{25}{16} = 3.125 \text{ W Ans}$$

Example 9

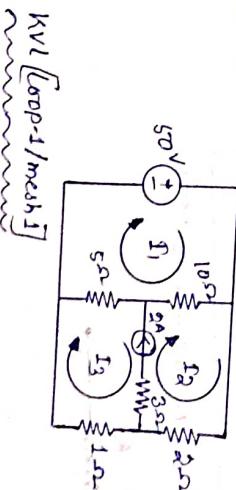

KVL (loop-1/mesh-1)

$$\Rightarrow -50 + (2I_1 - I_2) 10 + (I_1 - I_3) 5 = 0$$

$$\Rightarrow (2I_1 - I_2) 10 + (I_1 - I_3) 5 = 50 \quad \dots \text{①}$$

KVL (Sm)

$$\Rightarrow (I_2 - I_1) 10 + 2I_2 + I_3 + (I_3 - I_1) 5 = 0$$

$$\Rightarrow -15I_1 + 12I_2 + 6I_3 = 0 \quad \dots \text{②}$$

KCL

$$I_2 - I_3 = 2A \quad \dots \text{③}$$

Solving the above eqns

$$I_1 = 19.99A, I_2 = 17.33A, I_3 = 15.33A$$

→ The current in the $5\ \Omega$ resistor = $I_1 - I_3$

$$I_{5\Omega} = 19.99 - 15.83 = 4.16\ A$$

Nodal Analysis → (KCL + Ohm's law)

A nodal analysis is a technique used to find the voltage at various nodes of an electric circuit.

This can be done by using KCL at various nodes.

The application of KCL at each node will give the nodal equation.


In a N -node circuit, one of the nodes is chosen as reference or datum node, then it is possible to write $N-1$ nodal equations by assuming $N-1$ node voltage.

Note:-

The node voltage is the voltage of a given node w.r.t one particular node, called the reference node, which we assume at zero potential.

A node is a point in an electric circuit at which current divides.

Example

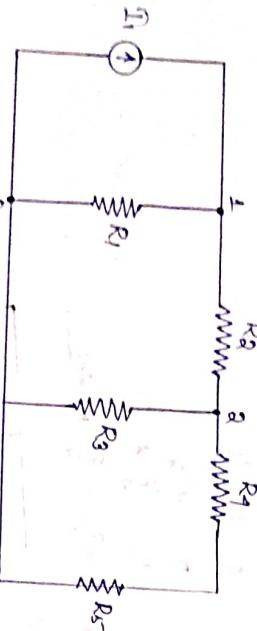

→ Node-3 is assumed as the reference node.

Voltage at node-1 i.e. (v_1)


$$\begin{aligned} &\text{Applying KCL at node } 1: \\ &\Rightarrow \frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2} = 0 \\ &\Rightarrow v_1 \left[\frac{1}{R_1} + \frac{1}{R_2} \right] - v_2 \left[\frac{1}{R_2} \right] = 0 \quad \dots \textcircled{1} \end{aligned}$$

$$\begin{aligned} &\text{Applying KCL at node } 2: \\ &\Rightarrow \frac{v_2 - v_1}{R_2} + \frac{v_2}{R_3} + \frac{v_2 - v_4}{R_4} = 0 \\ &\Rightarrow -v_1 \left[\frac{1}{R_2} \right] + v_2 \left[\frac{1}{R_3} + \frac{1}{R_4} + 1 \right] = 0 \quad \dots \textcircled{2} \end{aligned}$$

From solving this equation (1) and (2) we have

$$v_1 = 19.85V, v_2 = 16.9V$$
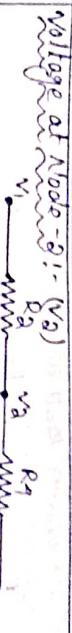
$$\begin{aligned} &\Rightarrow I_{1\Omega} = \frac{v_1}{R_1} = \frac{19.85}{10} = 1.985A \\ &\Rightarrow I_{3\Omega} = \frac{v_1 - v_2}{R_3} = \frac{19.85 - 16.9}{3} = 0.98A \\ &\Rightarrow I_{5\Omega} = \frac{v_2}{R_5} = \frac{16.9}{5} = 3.38A \\ &\Rightarrow I_{1\Omega} = \frac{v_2}{R_1} = 0.9A \end{aligned}$$



$$\begin{aligned} &\Rightarrow \frac{v_1 - v_1}{R_1} + \frac{v_1 - v_3}{R_2} + \frac{v_1 - v_3}{R_4} = 5 \\ &\Rightarrow -v_1 \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right] + v_3 \left[\frac{1}{R_2} + \frac{1}{R_4} \right] = 5 \quad \dots \textcircled{3} \end{aligned}$$

$$\begin{aligned} &\text{Applying KCL at node } 3: \\ &\Rightarrow \frac{v_3 - v_1}{R_2} + \frac{v_3 - v_5}{R_3} + \frac{v_3 - v_5}{R_5} = 0 \\ &\Rightarrow \frac{v_3 - v_1}{R_2} + \frac{v_3}{R_3} + \frac{v_3 - v_5}{R_5} = 0 \\ &\Rightarrow -v_1 \left[\frac{1}{R_2} \right] + v_3 \left[\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5} \right] = 0 \quad \dots \textcircled{4} \end{aligned}$$

From solving this equation (3) and (4) we have

$$\begin{aligned} &v_1 = 19.85V, v_3 = 16.9V \\ &\Rightarrow I_{1\Omega} = \frac{v_1}{R_1} = \frac{19.85}{10} = 1.985A \\ &\Rightarrow I_{3\Omega} = \frac{v_1 - v_3}{R_3} = \frac{19.85 - 16.9}{3} = 0.98A \\ &\Rightarrow I_{5\Omega} = \frac{v_3}{R_5} = \frac{16.9}{5} = 3.38A \end{aligned}$$

Model Equations by Inspection method

By comparing the eqs (1) and (5) with eqn (self conductance) = $(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3})^{-1}$

\Rightarrow sum of the conductances connected to node 'a'


Gab (negative conductance): $\tilde{z} = \frac{1}{2}$

Grab (cont'd) 35-Substrates (R₃)₂

17

卷之三

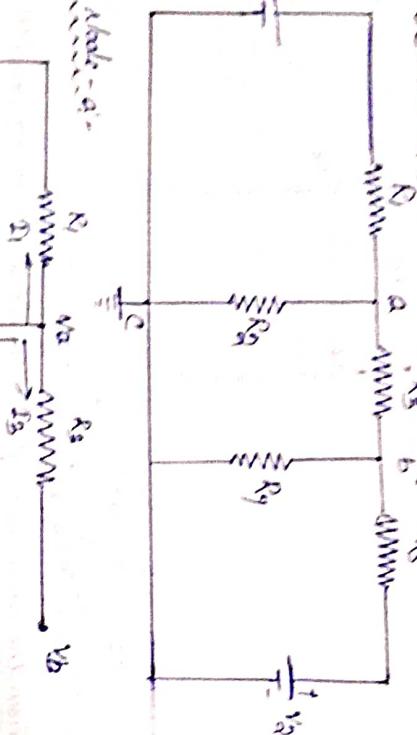A circuit diagram showing a series circuit with three resistors (R_1 , R_2 , R_3) connected in series between terminals A and B.



ΣI_1 and ΣI_2 are the sum of the super currents at the node 'a' and the node 'b' respectively.

Solve the node equation by inspection method.

1000

Solution:-

$$\Rightarrow \text{GraVa} + \text{GraVb} = 1 - \dots \quad \text{①}$$

$$\Rightarrow V_{\text{ba}} V_a + V_{\text{bb}} V_b = I_Q \quad \dots \quad \text{Q} \quad \text{E}$$

$$f_{\text{Gibb}} = \left(\frac{1}{1 + e^{-\frac{E}{kT}}} \right) = 1.832$$

卷之二

$$I_1 = \frac{10}{1} = 10 \text{ A}$$

دیوان
۱۳

$$1.83V_0 - 0.33V_B = 11$$

$$-0.33V_{\text{A}} + 1.03V_{\text{B}} = 1.83 \quad \dots \textcircled{2}$$

$$V_R \approx 6.023, \quad V_b \approx 3.125$$

Solomon

The general equation are,

⇒ $\text{GraVa} + \text{GraVb} = \text{In}$

$$G_{\text{pa}} = \left(\frac{1}{1} + \frac{1}{2} + \frac{1}{3} \right) = 1.83 \text{ sr}$$

$$f_{\text{bb}} = \left(\frac{1}{3} + \frac{1}{5} + \frac{1}{2} \right) = 1.03$$

وَمِنْهُمْ مَنْ يَعْمَلُ مُجْرِيًّا وَمَا يَعْمَلُ إِلَّا مَنْ

ج

Klaatal Equation.


$$-0.33\text{Va} + 1.03\text{Vb} = 1.83 \quad \text{(2)}$$

$$V_R \approx 6.023, \quad V_b \approx 3.125$$

Supernode Analysis :-

If the total voltage source (either independent or dependent) is connected between two non-reference nodes then those two non reference node is formed as generalized node or supernode.
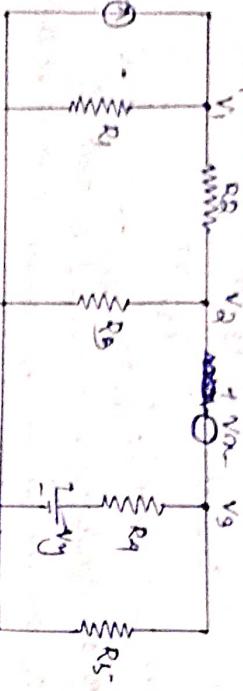
$$\text{Supernode} = \text{Net} + \text{KVL law} + 6V$$



Net at node 1 :-

$$I = \frac{V_1}{R_1} + \frac{V_1 - V_2}{R_2}$$

Due to presence of voltage source, V_{12} is between node 2 and 3, it is slightly difficult to find out the current so supernode technique can be conveniently in this case.


Net kvl at node 2 and 3 :-

$$\Rightarrow \frac{V_2 - V_1}{R_2} + \frac{V_2}{R_3} + \frac{V_3 - V_2}{R_4} + \frac{V_3}{R_5} = 0$$

Net at node 2 and 3

$$\Rightarrow V_2 - V_3 = V_A$$

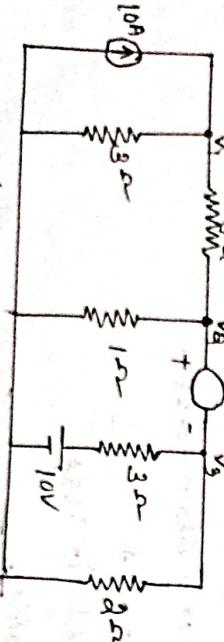Ex Determine the current in the 5Ω resistor for the circuit shown in below figure



Soln Net at node 1 :-

$$\Rightarrow 10 = \frac{V_1}{3} + \frac{V_1 - V_2}{2}$$

$$\Rightarrow V_1 \left(\frac{1}{3} + \frac{1}{2} \right) - \frac{V_2}{2} = 10 \Rightarrow 0.83V_1 - 0.5V_2 = 10 \quad \text{--- (1)}$$

kvl at Node 2 and Node 3 (by supernode eq)


$$\Rightarrow \frac{V_A - V_1}{2} + \frac{V_A}{1} + \frac{V_3 - 10}{5} + \frac{V_3}{3} = 0$$

$$\Rightarrow -0.5V_1 + 1.5V_2 + 0.7V_3 = 2 \quad \text{--- (2)}$$

$$\text{kvl at Node 2 and Node 3 :-} \\ V_2 - V_3 = 20 \quad \text{--- (3)}$$

$$\text{Solving eq (1) and (2) and (3) eqn} \\ V_1 = 19.03, V_2 = 11.59, V_3 = -2.10$$

Ex

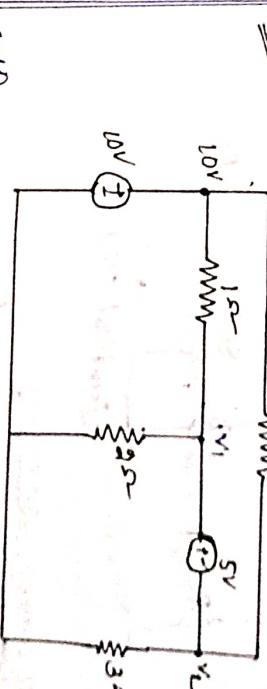

Soln

$$\frac{V_1 - 10}{1.5} + \frac{V_1}{2} = 0$$

$$\frac{V_A - 10}{4} + \frac{V_A}{3} = 0$$

$$\text{Net eqn } V_1 - V_2 = 5 \quad \text{--- (1)}$$

$$\frac{V_1 - 10}{1} + \frac{V_1}{2} + \frac{V_A - 10}{4} + \frac{V_A}{3} = 0$$

$$\Rightarrow V_1 \left(1 + \frac{1}{2} \right) + V_A \left(\frac{1}{4} + \frac{1}{3} \right) - 10 \left(\frac{4+1}{4} \right) = 0$$

$$\Rightarrow 1.5V_1 + 0.58V_A = 10.5 \quad \text{--- (2)}$$

Solving eqn (1) and (2)

$$V_1 = 7.40, V_A = 2.90$$

Source transformation technique

Voltage Source to Current Source :-




$$(Ideal \ I_s)$$

$$I_s = \frac{V_s}{R_L}$$


(practical I_s)

Current Source to Voltage Source :-

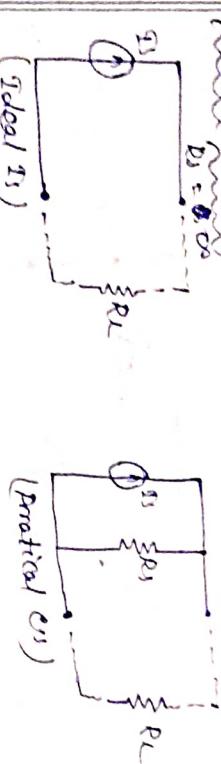

$$V_s = I_s R_L$$

Voltage Source to Current Source :-

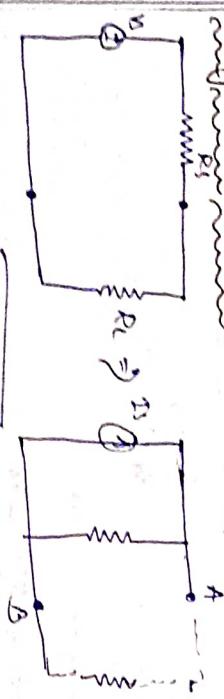

$$I_s = \frac{V_s}{R_L}$$

Current Source to Voltage Source :-



$$V_s = I_s R_L$$

Dependent Source :-

- can be transformed as direct as convert into dependent terminal to two terminal voltage source.
- Source transformation is valid for both independent as well as dependent practical source.
- Source transformation is not valid for ideal voltage source and ideal current source.


fig - vers

fig - vers

fig - vers

fig - vers

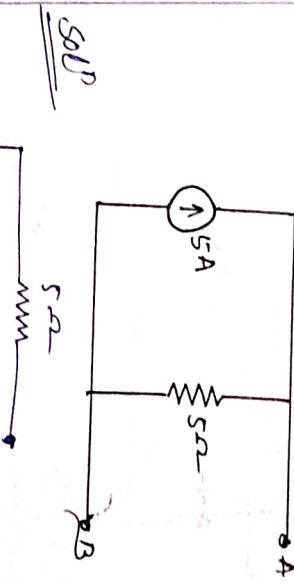
Example :- Determine the equivalent voltage source for the current source shown in fig.



SOL

$\Delta S \Delta (I_m)$

$$V_s = I_m R_s$$

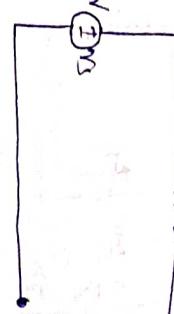

CHAPTER-4

Norton's theorems

Network theorems provides alternative approach for calculating ob' current and voltage in the network.


\Rightarrow we will discuss four network theorems.

- 1) Superposition Theorem
- 2) Thevenin Theorem
- 3) Norton's Theorem
- 4) Maximum Power Transfer Theorem.


Superposition Theorem:

It states that in a linear network containing more than one source If current in any branch the potential difference across any two points can be found by considering each source separately and then by adding their individual effect. While considering each source, the other sources are replaced by their internal resistances. If the value of internal resistance of the sources are not given, the voltage sources are (ideal) are short circuited and the current source (total) are open circuited.


Ex

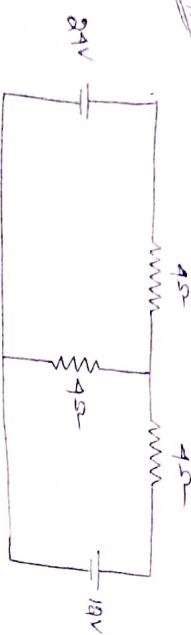

Step-1 consider 24V source

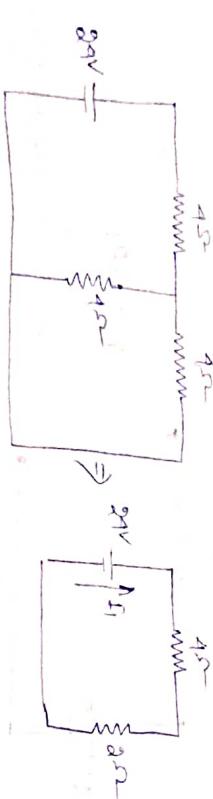


Step-2 consider 12V source

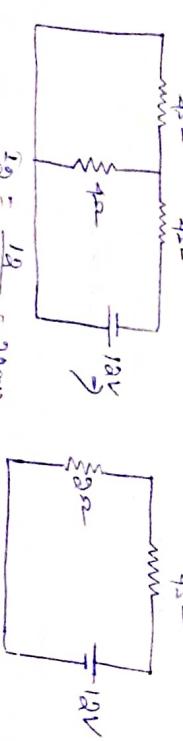

$$I_1 = \frac{24}{4.5 + 4.5} = 2 \text{ Amp}$$

$$I_2 = \frac{12}{4.5 + 4.5} = 1 \text{ Amp}$$

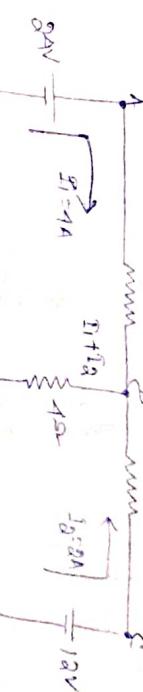
Now, we will combine the effect of the two voltage sources.



Current supplied by 24V source = 4 Amp
Current through the branch AB = 2 Amp
Current supplied by the 12V source = 3 Amp
Current through branch CD = 2 Amp
Current through branch BD = 6 Amp

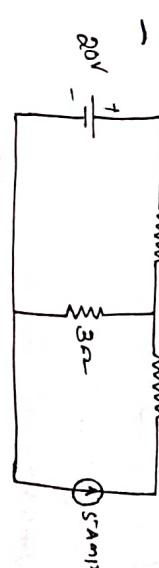Example

calculate the current through the 3Ω resistor by using superposition theorem.



Sol) The current due to the (20V) source with the 20V source short circuited is $I_1 = \frac{20}{5 + 3} = 2.5 \text{ Amp}$




$$I_1 = \frac{20}{5 + 3} = 2.5 \text{ Amp}$$

The current due to the 20V source with 20V source open circuit is. $I_2 = \frac{10}{3 + 10} = 0.769 \text{ Amp}$

$$I_2 = \frac{10}{3 + 10} = 0.769 \text{ Amp}$$

\Rightarrow the total current passing through the 3Ω resistor $I = (2.5 + 0.769) = 3.269 \text{ Amp}$.

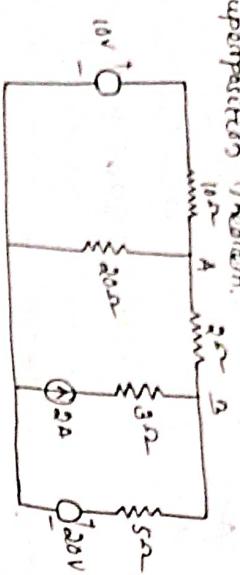Ex Calculate the voltage across the 2Ω resistor by using superposition theorem.



Step 1

Set 1
short
Voltage across the 2Ω resistor due to the 10V source while other sources are set equal to zero.



Assuming a voltage 'V' at the node point 'A',

$$\frac{V-10}{10} + \frac{V}{8} + \frac{V}{7} = 0$$

$$V(0.1 + 0.5 + 0.193) = 1$$

$$\Rightarrow V = 8.41V$$


→ Voltage across the 2Ω resistor due to the 10V source is

$$V_{12} = \frac{V}{7} \times 2 = 0.97V$$

Step 2
Voltage across the 2Ω resistor due to the 20V source, while the other sources are set equal to zero.

Set 2
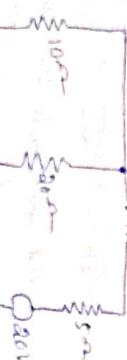
$$\frac{V-20}{9} + \frac{V}{8} + \frac{V}{7} = 0$$



$$\Rightarrow V(0.178 + 0.5 + 0.1) = 2.08V$$

$$\Rightarrow V = \frac{2.08}{0.273} = 7.56V$$

→ The voltage across the 2Ω resistor due to the 20V source is

$$V_{21} = \frac{V-20}{7} \times 2 = -2.92V$$

Step 3

Voltage across the 2Ω resistor due to the 20V current source while other source are set equal to zero.

The current in the 2Ω resistor,

$$= 2 \times \frac{5}{5+8.57} \\ = \frac{10}{13.67} = 0.73A$$



voltage across the 2Ω resistor = $0.73 \times 2 = 1.46V$
The algebraic sum of those voltage gives the total voltage across the 2Ω resistor in the network.

$$V = 0.97 - 0.92 - 1.46 \\ = -3.41V$$


-ve sign indicates that the voltage at 'A' is negative.

Thevenin's theorem!

It states that "any two terminal linear having a no. of voltage & current sources and resistances can be replaced by a simple equivalent circuit consisting of a single voltage source in series with a resistance where, the value of the voltage source is equal to the open circuit voltage across the two terminals of the network and resistance is equal to the equivalent resistance measured before the terminals with all the energy sources are replaced by their internal resistance".

Example

Step 1

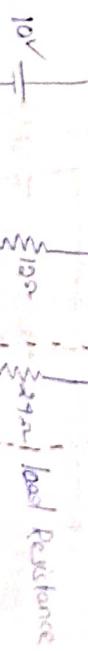

Step 2



10Ω load Resistance



Step 3

In the circuit, 2Ω load resistance is connected to Thevenin's equivalent open circuit.
Thevenin voltage is equal to the DC voltage across the terminal AB in the voltage across the 10Ω resistance when the load resistance is disconnected from the circuit, the cut, the Thevenin voltage

$$V_{TH} = V_{OC} = 10 \times \frac{10}{10+2} = 8.33V$$

The resistance into the o.c terminals is equal to the R_{TH}

$$R_{TH} = \frac{10 \times 2}{10+2} = 1.73\Omega$$

Now find the current passing through the R_{AB} resistance and voltage across it due to Thevenin's equivalent cell.

$$I_{AB} = \frac{V_{TH}}{R_{AB}} = 0.33A$$

$$V_{AB} = 50 - 16.7 = 33.3V$$



Voltage across the R_{AB} resistance is equal to $V_{AB} = 0.33 \times 33A = 7.92V$

In General method

$$I_{AB} = I_T \times \frac{10}{R_{AB}}$$


$$I_T = \frac{10}{3 + (10/12)} = \frac{10}{10} = 1Amp$$

$$I_{AB} = 1 \times \frac{10}{10+12} = 0.33A$$

$$V_{AB} = 0.33 \times 33A = 7.92V$$

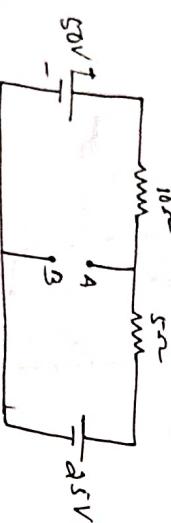Example

Determine the Thevenin's equivalent circuit across 'AB' for the given cut shown in below



To solve first V_{TH} -



$$\Rightarrow 50 - 25 = 10I + 5I \Rightarrow$$

$$\Rightarrow \frac{25}{15} = 2I = 1.67Amp$$

Voltage across $R_{AB} = 10 \times 1.67 = 16.7V$

$$V_{AB} = V_{TH} = 50 - 16.7 = 33.3V$$


$$V_{TH} = 50 - 16.7 = 33.3V$$

Find R_{TH} -

Two voltage sources are removed & replaced with short circuit. The resistance at terminal AB is


$$R_{TH} = \frac{10 \times 5}{10+5} = 3.33\Omega$$

The equivalent Thevenin cut is

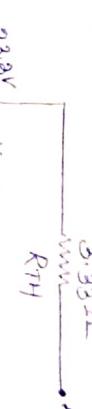

Norton Theorem -

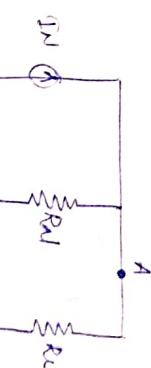It state that, "Any two terminal linear network with current sources, voltage sources and resistance can be replaced by an equivalent circuit consisting of a current source in parallel with a resistance.



(Norton Equivalent cut)


∴ Norton current is referred also current across the load terminals.

That mean voltage across load terminal is zero.

$$(dV = 0)$$

Norton resistance is same as Thevenin resistance.

Example

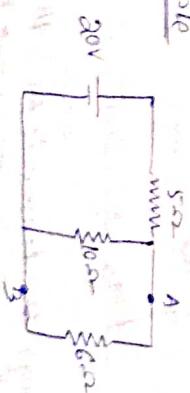

$$R_{TH} = R_{AB}$$

$$R_{TH} = R_{AB}$$


For I_{nl}

$$I_{nl} = \frac{30}{5}$$


$$I_{nl} = 6$$

For R_{nl}
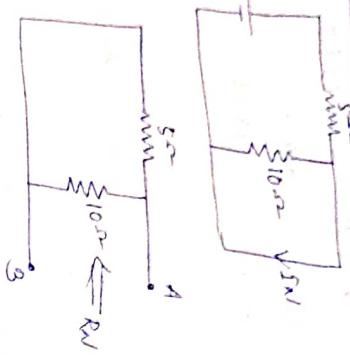
$$R_{nl} = \frac{5 \times 10}{5+10} = 3.33 \Omega$$



Norton Equivalent cut

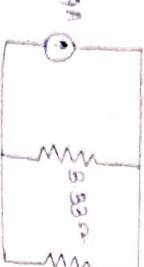


$$I_{C,2} = 4 \times \frac{3.33}{6+3.33} = 1.93 \text{ Amp}$$

→ voltage across the 6 ohm resistor
 $= 1.93 \times 6 = 8.58 \text{ volt}$

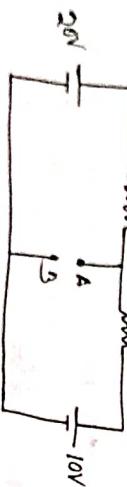
Example

Determine Norton's equivalent cut at terminal AB for the circuit shown in below figure.



Sol:

Norton's equivalent cut

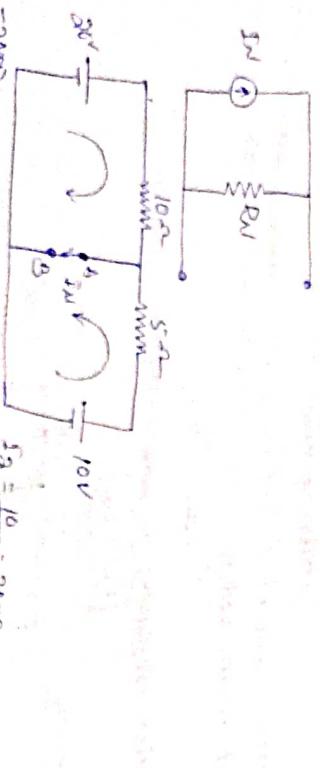

Sol:

Norton's equivalent cut

Norton's equivalent cut

The current passing through the terminals AB is I_A .

$$I_A = \frac{20}{10} = 2 \text{ Amp}$$

$$I_A = \frac{10}{5} = 2 \text{ Amp}$$

→ The current passing through the terminals AB is I_A .

$$I_A = \frac{20}{10+5} = 1.33 \text{ Amp}$$


$$I_A = \frac{10}{10+5} = 2 \text{ Amp}$$

Maximum Power Transfer Theorem:-

The power is supplied from the source to the load.

Let assume the internal resistance or source resistance or the source be R_S and the load no resistance be R_L . The cut will be

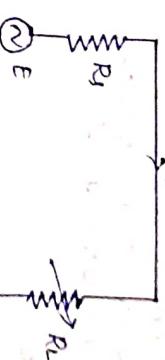source to R_S and the load no resistance be R_L . The cut will be



(Source)

(load)

⇒ From npt, we find out at what value of load (load resistive) maximum power will be transferred from the source to the load.

⇒ The current flowing in the cut is given as follows:-

$$I = \frac{E}{R_S + R_L}$$

⇒ Power delivered is equal to power consumed assuming nothing less. Power delivered (P) is expressed as

$$P = I^2 R_L = \left(\frac{E}{R_S + R_L} \right)^2 R_L = \frac{E^2 R_L}{(R_S + R_L)^2}$$

⇒ To determine the value of R_L at which P will be maximum, we differentiate P with respect to R_L and equate to zero.

$$\frac{dP}{dR_L} = \frac{d}{dR_L} \left[\frac{E^2 R_L}{(R_S + R_L)^2} \right] = 0$$

$$\Rightarrow \frac{d}{dR_L} E^2 [R_L (R_S + R_L)^{-2}] = 0$$

$$\Rightarrow E^2 \left[1(R_S + R_L)^{-3} + R_L (-2)(R_S + R_L)^{-4} \right] = 0$$

$$\Rightarrow E^2 \left[\frac{1}{(R_S + R_L)^3} - \frac{2R_L}{(R_S + R_L)^4} \right] = 0$$

$$\Rightarrow (R_S + R_L)^2 - 2R_L = 0$$

$$\Rightarrow R_S - R_L = 0$$

$$\Rightarrow R_S = R_L$$

∴ we can conclude that the maximum power will be transferred when the value of load resistance is equal to the source resistance or load resistance becomes equal to the source.

∴ maximum power is transferred to the load when load resistance is equal to the source resistance. So, the value of maximum power is calculated as follows:

$$\Rightarrow P_{max} = E^2 R_L$$

$$\Rightarrow P_{max} = \frac{E^2 R_L}{(R_L + R_s)^2} = \frac{E^2 R_L}{R_L^2 + 2R_s R_L + R_s^2}$$

$$\Rightarrow P_{max} = \frac{E^2}{R_L + R_s} \quad (\text{where } R_s = R_L)$$

∴ short circuiting power is (P_{sc}) = $E^2 R_s$

∴ open circuit power is (P_{oc}) = $E^2 R_L$

$$\Rightarrow P_{oc} = \frac{E^2 R_L}{R_L + R_s}$$

∴ maximum power delivered

$$P_{max} = \frac{E^2 R_L}{R_L + R_s}$$


$$\boxed{P_{max} = \frac{E^2}{R_L + R_s}}$$

percentage efficiency (η) = $\frac{P_{max}}{P_{sc}} \times 100$

$$\boxed{\eta = \frac{E^2 / R_L}{E^2 / R_s} \times 100}$$

$$\boxed{12.5\%}$$

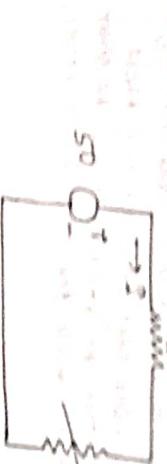Example 5: Determine the value of load resistance when the load resistance draws maximum power. Also find the value of the max power.



Sol: Equivalent circuit




∴ source delivers the maximum power when load resistance equals to the source resistance.

$$R_s = 5\Omega \text{ so } R_L = 5\Omega$$

$$I = \frac{50}{5+5} = 5A$$

$$\therefore P_{max} = 5^2 \times 5 = 125W$$

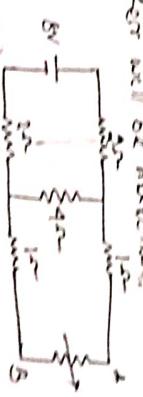Ex: A 6V battery is supplying power through resistors to a load as shown in fig. Calculate the value of R_L at which the power transferred will be maximum.




Sol: The circuit is converted into a Thévenin equivalent circuit as shown below

$$\text{fig. 111} \quad \boxed{R_s = \frac{6}{2+4} = 1\Omega}$$

$$V_{TH} = 6 - 4 \times 1 = 2V$$
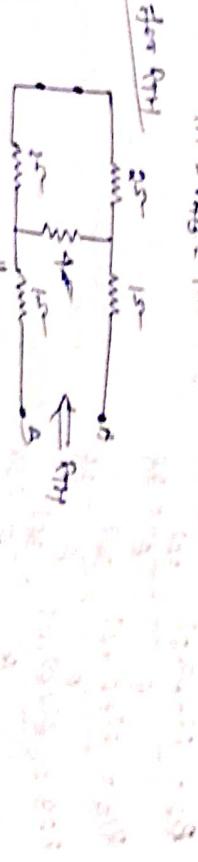
$$\text{Now } R_L = \frac{V_{TH}}{I} = \frac{2}{2} = 1\Omega$$



$$2A \quad \frac{2}{2} = 1\Omega \quad \Leftrightarrow R_L = 2+1=1=1\Omega$$

STAR - DELTA TRANSFORMATION:-

- ⇒ This transformation technique is useful in solving complex networks.
- ⇒ Any three ohm elements, i.e. resistive, inductive, capacitive may be connected in two different ways. One way of connecting these elements is called the star connection or Y-connection. The other way of connecting these elements is called the delta(Δ) connection.

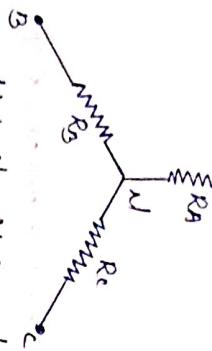


Fig:- Star Y connection

when the resistors are neither in series nor in parallel connection, these type of circuit can be simplified by using 3-terminal equivalent network (Y or A connection).

In case of star - delta conversion, the same impedance increases the impedance by factor of 3.

Star to delta conversion:-

$$R_{12} = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_{13} = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$R_{23} = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_1 = R_1 + R_2 + R_3$$

$$R_2 = R_1 + R_2 + R_3$$

$$R_3 = R_1 + R_2 + R_3$$

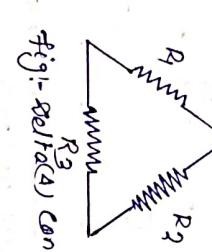


Fig:- Delta(Δ) connection

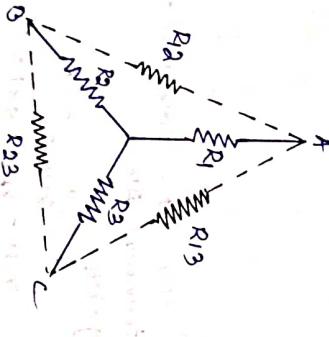



Fig:- Star to Delta(Δ) conversion

Delta to star conversion :-

$$R_1 = \frac{R_{12} \cdot R_{23}}{R_{12} + R_{13} + R_{23}}$$

$$R_2 = \frac{R_{12} \cdot R_{13}}{R_{12} + R_{13} + R_{23}}$$

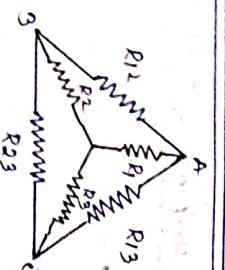
$$R_3 = \frac{R_{13} \cdot R_{23}}{R_{12} + R_{13} + R_{23}}$$



⇒

In delta to star conversion, the same impedance decreases impedance by factor of 3.

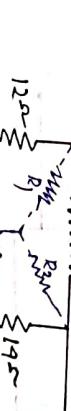Ex:- obtained the star-connected equivalent for the delta connected circuit.



$$\text{SOLN:- } R_1 = \frac{12 \times 13}{12 + 13 + 19} = 9\Omega$$

$$R_2 = \frac{13 \times 19}{12 + 13 + 19} = 4.66\Omega$$

$$R_3 = \frac{14 \times 19}{12 + 13 + 19} = 4.31\Omega$$

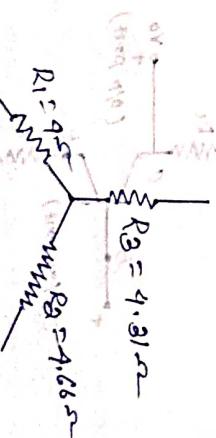


Fig:- Star to Delta(Δ) conversion

$$R_1 = 9\Omega \quad \text{using } R_1 = 9\Omega$$

$$R_2 = 4.66\Omega$$

$$R_3 = 4.31\Omega$$

Two Port Network

Termination - A pair of terminal at which a signal may either enter or leave network is called a port.




One port n/w - The pair of terminal n/w is referred as one port n/w.




Half - Generator, motor etc. (fig:- One port n/w)

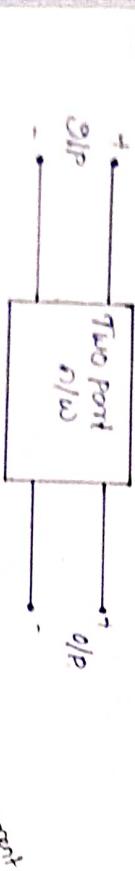Two port n/w - Two pairs of terminal n/w is referred as two port n/w.



Opposite current

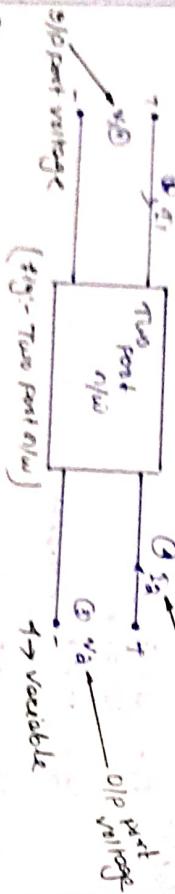

Opposite voltage (S/P - Two port n/w)


Ex :- Transformer -



Opportunities -

Opportunities -

Representation of two port n/w

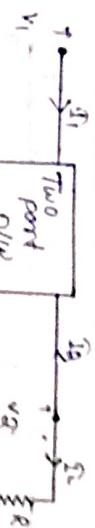

$$V_1 = Z_{11} I_1$$

I_L = load current
 I_2 = O/P port current.

Maximum no. of possible parameter in 2 port n/w is.

$$N_0 = N_m$$

$$N_0 = N_m = 4C_2 = \frac{4!}{2!(4-2)!} = \frac{24}{2 \cdot 2 \cdot 2!} = 6$$

$$S/P \quad O/P$$

\rightarrow \rightarrow \rightarrow \rightarrow \rightarrow \rightarrow

$AECO$ parameter

b -parameter

y -parameter

Z -parameter

\rightarrow \rightarrow \rightarrow \rightarrow \rightarrow \rightarrow

$(AECO)^T$ parameter

Z-parameter (Impedance Parameter) :-

$$(S/P n/w) \quad V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \dots \dots \dots \quad (1)$$

$$(O/P n/w) \quad V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \dots \dots \dots \quad (2)$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$


$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

Independent variables :- I_1, I_2
Dependent variables :- V_1, V_2

Condition for existence of Z -parameter :-
Number of independent variables ≥ 2

- I_1 and I_2 should be independent from each other.
- If I_1 and I_2 are dependent then Z -parameter does not exist.

Impedance model:-

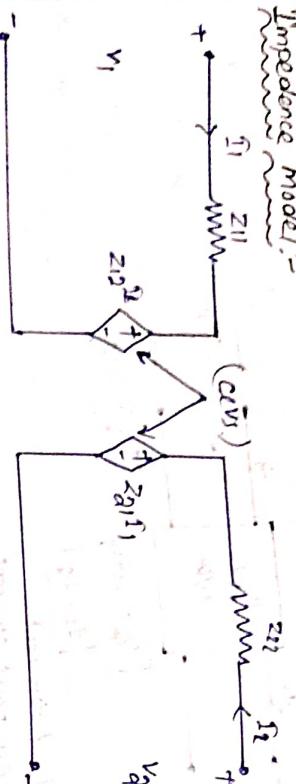

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \dots \quad (1)$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad \dots \quad (2)$$

$Z_{11} = \frac{V_1}{I_1} \mid I_2=0$ Driving point G/P impedance when O/P = 0.c


$Z_{22} = \frac{V_2}{I_2} \mid I_1=0$ Transfer I/P impedance when O/P = 0.c

$Z_{12} = \frac{V_2}{I_1} \mid I_2=0$ Transfer O/P impedance when O/P = 0.c

Symmetrical condition:-

For Symmetrical condition $[Z_{12} = Z_{21}]$

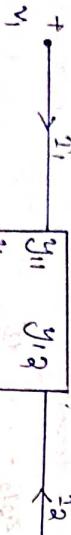Y-parameter and short cut parameter and Admittance parameter



Condition for reciprocity :- $[Y_{12} = Y_{21}]$

Condition for Symmetry :- $[Y_{11} = Y_{22}]$

Conversion from Z-parameter to Y-parameter:-

$$[Y]_{2x2} = [Z]_{2x2}^{-1} [Z]_{1x1}$$

$I_1 = Z_{11}V_1 + Z_{12}V_2$ Independent variable = V_1, V_2


$I_2 = Z_{21}V_1 + Z_{22}V_2$ Dependent variable = I_1, I_2

Condition for writing of Y parameter:-

V_1 and V_2 should be independent at each other.

If V_1 and V_2 are dependent then Y-parameter doesn't exist.

Admittance Model:-

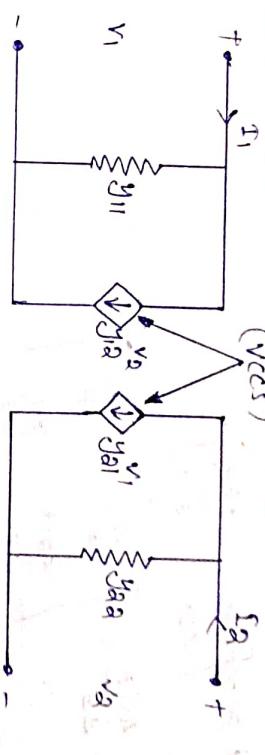

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

Y-parameter Element:-

$Y_{11} = \frac{I_1}{V_1} \mid V_2=0$ Driving point I/P admittance when O/P = s.c

$Y_{22} = \frac{I_2}{V_2} \mid V_1=0$ Transfer I/P admittance when O/P = s.c

$Y_{12} = \frac{I_2}{V_1} \mid V_2=0$ Transfer O/P admittance when O/P = s.c

$Y_{21} = \frac{I_1}{V_2} \mid V_1=0$ Driving point O/P admittance when I/P = s.c

Y-parameter is preferred as short-cut parameter because in all calculation we consider either I/P I.s.c or O/P is s.c.

Condition for reciprocity :- $[Y_{12} = Y_{21}]$

Condition for Symmetry :- $[Y_{11} = Y_{22}]$

Conversion from Z-parameter to Y-parameter:-

$$[Y]_{2x2} = [Z]_{2x2}^{-1} [Z]_{1x1}$$

$$[T_2] = [V_2][T_1]$$

$$[T_2]_{2 \times 2} = \begin{bmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{bmatrix}$$

Determinant $A_2 = T_{11}T_{22} - T_{12}T_{21}$

$$\text{dependent } Z = \begin{bmatrix} T_{22} \\ T_{21} \end{bmatrix} - T_{12}.$$

$$[T_2]^{-1} = \frac{A_2}{A_2^2} = \begin{bmatrix} T_{22} & -T_{12} \\ -T_{21} & T_{11} \end{bmatrix}$$

$$[Y_2] = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}$$

$$Y_{11} = \frac{T_{22}}{A_2}, \quad Y_{21} = \frac{-T_{12}}{A_2}, \quad Y_{12} = \frac{T_{21}}{A_2}, \quad Y_{22} = \frac{T_{11}}{A_2}$$

Conversion from Y-parameter to Z parameter:-

$$[T_1]_{2 \times 2} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} [T_1]$$

$$[T_1]_{2 \times 1} = [V_1 \quad V_2]$$

$$[V_1]_{2 \times 1} = [V_{11} \quad V_{12}]$$

$$[V_2]_{2 \times 1} = [V_{21} \quad V_{22}]$$

$$[V_1]_{2 \times 1} = [V_{11} \quad V_{12}]$$

$$Adi_1 = \begin{bmatrix} V_{11} & V_{12} \\ V_{21} & V_{22} \end{bmatrix}$$

$$Adi_2 = \begin{bmatrix} V_{12} \\ V_{21} \end{bmatrix}$$

$$\begin{bmatrix} V_{11} \\ V_{21} \end{bmatrix} = \begin{bmatrix} \frac{V_{11}}{A_2} & \frac{-V_{12}}{A_2} \\ \frac{-V_{21}}{A_2} & \frac{V_{22}}{A_2} \end{bmatrix}$$


$$[T_1] = \begin{bmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{bmatrix}$$

$$V_1 = \frac{V_{11}}{A_2}, \quad V_{12} = \frac{-V_{12}}{A_2}, \quad V_{21} = \frac{-V_{21}}{A_2}, \quad V_{22} = \frac{V_{22}}{A_2}$$

Hybrid parameter (H parameter) :-

H-parameter is used for analysis at two frequency i.e. O.P. & I.P. $V_{11} = V_{11}(0)$, $V_{12} = V_{12}(0)$, $V_{21} = V_{21}(0)$, $V_{22} = V_{22}(0)$.

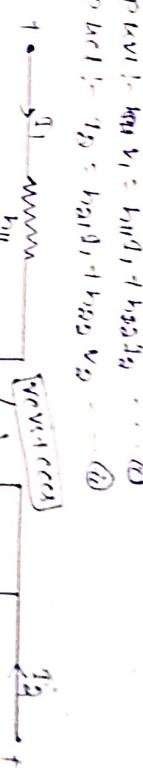I.P. $V_{11} = V_{11}(0)$, $V_{12} = V_{12}(0)$, $V_{21} = V_{21}(0)$, $V_{22} = V_{22}(0)$.



V_1


V_{11}, V_{12}

V_2

(H-parameter)
Independent variable = V_1, V_2
Dependent variable = V_1, V_2

$V_1 = f(C_1, C_2)$
 $C_1 > f(C_1, V_2)$
for existence of H-parameter $V_1, \Delta V_2$ should be independent from each other.

$h_{11} = \frac{V_1}{V_1}|_{V_2=0}$ driving point input impedance where O.P. = s.c.

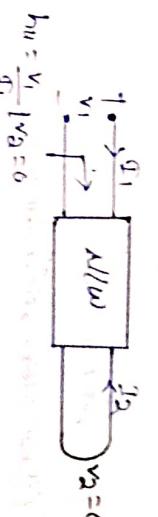

$h_{11} = \frac{V_1}{V_1}|_{V_2=0}$

h₁₂ = $\frac{V_1}{V_2}|_{V_1=0}$ = Reverse voltage gain when O.P. = 0.c.

h₂₁ = $\frac{V_2}{V_1}|_{V_2=0}$ = forward current gain when O.P. = 0.c.

h₂₂ = $\frac{V_2}{V_2}|_{V_1=0}$ = driving point o.p. admittance when O.P. = 0.c.

$$[h]_{2 \times 2} = \begin{bmatrix} h_{11}(t_1) & h_{12} \\ h_{21} & h_{22}(t_2) \end{bmatrix}_{2 \times 2}$$

Condition:-
Reciprocity:- $h_{12} = -h_{21}$

Symmetry:- $h_{11} = h_{22}$

$$[h] = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$$

$$\Delta h = h_{11}h_{22} - h_{12}h_{21}$$

ABC parameter or Transmission parameter:-

ABC parameter is used for transient analysis of transmission line.



$$S/P \text{ volt } - V_1 = AV_2 + BT_2$$

$$S/P \text{ curr } I_1 - T_1 = CV_2 + DV_2$$

$$(Both \text{ volt } \text{ and curr } \text{ exist at some time})$$

$$V_1 = AV_2 - BT_2$$

$$T_1 = CV_2 - DV_2 \quad (\text{Reverse current gain})$$

$$B = -\frac{V_1}{V_2} \quad (\text{Transistor Impedance})$$

$$C = \frac{I_1}{V_2} \quad (\text{Transistor Admittance})$$

$$D = -\frac{T_1}{V_2} \quad (\text{Current gain})$$

$$\text{Condition:-}$$

$$\text{Reciprocity: } A = D = 1$$

$$\text{Symmetry: } A = D = 1$$

ABC Parameter in terms of Z-parameter and γ -parameter:-

$$V_1 = AV_2 - BS_2 ; V_2 = B_1T_1 + B_2T_2 ; T_1 = Y_{11}V_1 + Y_{12}V_2$$

In Z-Parameter:-

$$(i) A = \frac{V_1}{V_2} | T_2 = 0$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \rightarrow 0$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$A = \frac{V_1}{V_2} = \frac{Z_{11}I_1}{Z_{21}I_1} = \frac{Z_{11}}{Z_{21}}$$

$$(ii) B = \frac{-V_1}{V_2} | V_2 = 0$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \rightarrow (1)$$

$$Z_{21}I_1 + Z_{22}I_2 \rightarrow (2)$$

$$Z_{21}I_1 = -Z_{22}I_2$$

$$I_1 = -\frac{Z_{22}}{Z_{21}}I_2$$

Put the equation (1)

$$\Rightarrow V_1 = Z_{11} \times \frac{-Z_{22}}{Z_{21}} I_2 + Z_{12}I_2$$

$$\Rightarrow -V_1 = \left(\frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{21}} \right) I_2 = \frac{A_2}{Z_{21}} \times I_2$$

$$B = -\frac{V_1}{V_2} = \frac{A_2}{Z_{21}}$$

$$(iii) C = \frac{I_1}{V_2} | T_2 = 0$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \rightarrow 0$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$\Rightarrow \frac{V_2}{I_1} = Z_{21}$$

$$\Rightarrow \frac{I_1}{V_2} = \frac{1}{Z_{21}} = C$$

$$\Rightarrow \frac{V_2}{I_2} = \frac{1}{Z_{21}} + Z_{22} = 0$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$= -Z_{22}I_1 = Z_{21}I_2$$

$$\Rightarrow I_2 = -\frac{Z_{21}}{Z_{22}}I_1$$

$$\Rightarrow I_2 = -\left(-\frac{Z_{21}}{Z_{22}} \right) = \frac{Z_{21}}{Z_{22}}$$

$$\left[\begin{matrix} A & B \\ C & D \end{matrix} \right] = \left[\begin{matrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{matrix} \right]$$

$$\left[\begin{matrix} A & B \\ C & D \end{matrix} \right] = \left[\begin{matrix} 1 & \frac{Z_{12}}{Z_{22}} \\ \frac{Z_{21}}{Z_{22}} & 0 \end{matrix} \right]$$

To h-Parameter:

$$A = \frac{V_1}{I_1} / I_2 = 0$$

$$\Rightarrow I_1 = V_1V_{11} + V_2V_{12} -$$

$$\Rightarrow I_2 = V_1V_{21} + V_2V_{22} -$$

$$\Rightarrow C = V_1 = V_2V_{11} + V_1V_{22} -$$

$$\Rightarrow B = \frac{V_1}{V_2} = -\frac{V_1V_{21}}{V_2V_{12}} = B$$

(ii)

$$I_2 = V_1V_{11} + V_2V_{12} = 0$$

$$\Rightarrow \frac{V_2}{I_1} = V_2I_1$$

$$\Rightarrow \frac{V_2}{I_1} = \frac{1}{V_1} =$$

$$= V_1 =$$

$$= V_1 = \frac{V_1V_{11} + V_2V_{12}}{V_2V_{11} + V_1V_{12}}$$

$$\Rightarrow \frac{V_1}{V_2} = -\frac{V_1V_{12}}{V_2V_{11}} = 1$$

(i)

$$A = \frac{V_1}{I_1} / I_2 = 0$$

To h-Parameter:

$$V_1 = V_1V_{11} + V_2V_{12}$$

$$\Rightarrow V_1 = V_1V_{11} + V_2V_{12} -$$

$$\Rightarrow V_2 = -V_1V_{12} / V_1 = -V_1V_{12}$$

$$\Rightarrow V_2 = -V_1V_{12} / V_1 = -V_1V_{12}$$

$$\Rightarrow V_2 = -V_1V_{12} / V_1 = -V_1V_{12}$$

(ii)

$$\Rightarrow I_1 = -\left(\frac{V_1V_{12}}{V_1V_{11} + V_2V_{12}} \right) V_2$$

$$\Rightarrow I_1 = -\frac{V_1V_{12}}{V_1V_{11} + V_2V_{12}} V_2$$

$$\Rightarrow I_2 = -\frac{V_1}{V_1V_{11} + V_2V_{12}} V_1$$

$$\left[\begin{matrix} A & B \\ C & D \end{matrix} \right] = \left[\begin{matrix} -\frac{V_1V_{12}}{V_1V_{11} + V_2V_{12}} & V_2 \\ -\frac{V_1}{V_1V_{11} + V_2V_{12}} & V_1 \end{matrix} \right]$$

To h-Parameter:

$$A = \frac{V_1}{I_1} / I_2 = 0$$

$$V_1 = V_1V_{11} + V_2V_{12}$$

$$\Rightarrow V_1 = V_1V_{11} + V_2V_{12} -$$

$$\Rightarrow V_2 = -V_1V_{12} / V_1 = -V_1V_{12}$$

$$C = \frac{I_1}{V_2} / I_2 = 0$$

$$\Rightarrow I_1 = V_1V_{11} + V_2V_{12}$$

$$\Rightarrow V_2 = V_1V_{11} + V_2V_{12}$$

$$\Rightarrow I_1 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

$$\Rightarrow I_2 = -V_1V_{11}X - V_2V_{12}Y + V_2V_{11}X + V_1V_{12}Y$$

(iv)

$$B = -\frac{V_1}{I_2} \mid V_2 = 0$$

$$V_1 = h_{11}I_1 + h_{12}V_2 \quad 0$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \quad 0$$

$$\Rightarrow -\frac{V_1}{I_2} = -\frac{h_{11}I_1}{h_{22}V_2} = -\frac{h_{11}}{h_{22}} = B$$

(v)

$$C = \frac{I_1}{V_2} \mid I_2 = 0$$

$$I_2 = h_{11}I_1 + h_{12}V_2$$

$$= 0 = h_{11}I_1 + h_{12}V_2$$

$$\Rightarrow -h_{11}I_1 = h_{12}V_2$$

$$\Rightarrow \frac{I_1}{V_2} = -\frac{h_{12}}{h_{11}} = C$$

(vi)

$$Z = \frac{-V_1}{I_2} \mid V_2 = 0$$


$$I_2 = h_{11}I_1 + h_{12}V_2 \quad 0$$

$$\frac{I_1}{I_2} = \frac{-1}{h_{11}} = Z$$

$$\boxed{Z_{21} = Z_b}$$

$$\boxed{Z_{22} = Z_b + Z_c}$$

$$\boxed{Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}}$$

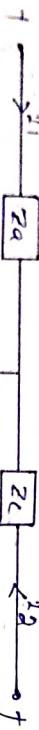T and π representation! -

T/P w/r

$$-V_1 + Z_{11}I_1 + Z_{12}(I_1 + I_2) = 0$$

$$\Rightarrow +V_1 = +(Z_{11} + Z_{12})I_1 + Z_{12}I_2 \quad 0 \quad \dots \textcircled{1}$$

$$\underline{\text{C/P w/r}}$$

$$-V_2 + Z_{21}I_1 + Z_{22}(I_1 + I_2) = 0$$

$$\Rightarrow V_2 = (Z_{21} + Z_{22})I_2 + Z_{22}I_1 \quad \dots \textcircled{2}$$

Comparing eq' \textcircled{1} & \textcircled{2} we get

$$Z_{11} = 30, Z_{12} = 20$$

$$\boxed{\begin{bmatrix} 30 & 20 \\ 20 & 50 \end{bmatrix}}$$

Comparision form standard Z parameter eq'!

$$V_1 = (Z_{11} + Z_{12})I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + (Z_{21} + Z_{22})I_2$$

$$\boxed{\begin{bmatrix} Z_{11} = 20 + Z_b \\ Z_{21} = Z_b \end{bmatrix}}$$

Example:-

$$\boxed{Z_{21} = 20}$$

$$\boxed{Z_{22} = 20 + 20}$$

$$\boxed{Z = \begin{bmatrix} Z_{11} + Z_{12} & Z_{12} \\ Z_{21} & Z_{21} + Z_{22} \end{bmatrix}}$$

Sol'
 $V_1 = 10I_1 + 20(I_1 + I_2)$

$$\Rightarrow V_1 = 10I_1 + 20I_1 + 20I_2$$

$$\Rightarrow V_1 = 30I_1 + 20I_2 \quad \textcircled{1}$$

Then

$$V_2 = 30I_2 + 20(I_1 + I_2)$$

$$\Rightarrow V_2 = 30I_2 + 20I_1 + 20I_2$$

$$\Rightarrow V_2 = 20I_1 + 50I_2 \quad \textcircled{2}$$

Z-parameter! -

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \textcircled{3}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad \textcircled{4}$$

Comparing eq' \textcircled{3} & \textcircled{4} we get



Put Vol at 1 -

$$-\gamma_1 + \gamma_B v_1 + \gamma_A (V_1 - V_2) = 0$$

$$\Rightarrow I_1 = \gamma_B v_1 + \gamma_A V_1 - \gamma_A V_2$$

$$\Rightarrow I_1 = y_1 (y_2 + y_3) - v_2 y_2 - \dots \quad (i)$$

Put Vol at 2 -

$$-v_2 + \gamma_C v_2 + \gamma_A (y_2 - y_1) = 0$$

$$\Rightarrow V_2 = \gamma_C v_2 + \gamma_A y_2 - \gamma_A y_1 \quad (ii)$$

$$\text{Then, } I_2 = \gamma_B v_1 + \gamma_A v_2 - \dots \quad (iii)$$

$$I_2 = \gamma_A v_1 + \gamma_B v_2 - \dots \quad (iv)$$

Compare eqn (i) & (ii) we get



$$[y_{11} = \gamma_B + \gamma_A \text{ & } y_{12} = -\gamma_A]$$

Compare eqn (iii) & (iv) we get

$$[y_{21} = -\gamma_A \text{ & } y_{22} = \gamma_B + \gamma_C]$$

$$Y = \begin{bmatrix} \gamma_B + \gamma_A & -\gamma_A \\ -\gamma_A & \gamma_B + \gamma_C \end{bmatrix}$$

Ex

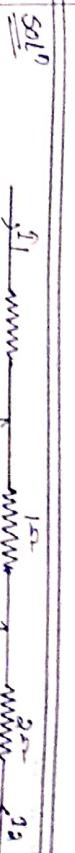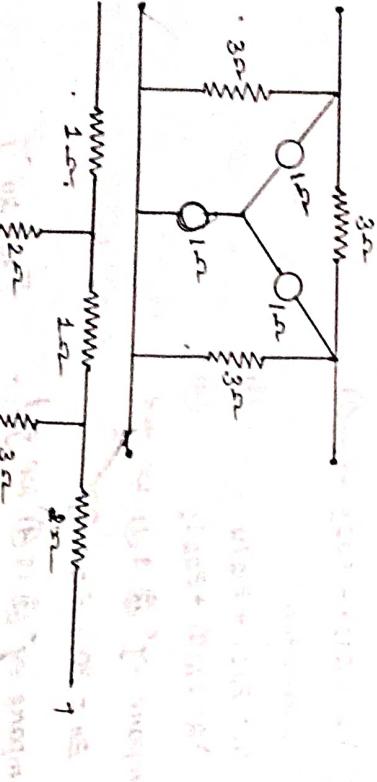

Convert π to star connection

$$R_1 = \frac{1 \times 3}{1+2+3} = \frac{2}{6} = \frac{1}{3}$$

$$R_2 = \frac{2 \times 3}{1+2+3} = \frac{6}{6} = 1$$

$$R_3 = \frac{3 \times 1}{1+2+3} = \frac{3}{6} = \frac{1}{2}$$


1st/3rd are series then

$$1 + \frac{1}{3}$$

$$= \frac{4}{3}$$

1/2 3/2 are series then

$$\frac{1}{2} + 1 = \frac{5}{2}$$

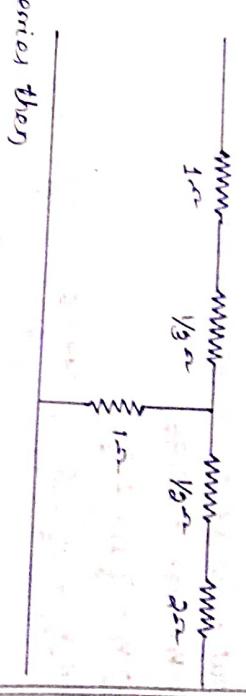

(5) "T" parameter to "Z" parameter

$$Z_{11} = \gamma_B + 1 = \frac{\gamma_B}{2} \quad Z_{12} = 1 \quad Z_{21} = 1 \quad Z_{22} = \frac{5}{2} + 1 = \frac{7}{2}$$

$$Z = \begin{bmatrix} \frac{\gamma_B}{2} & 1 \\ 1 & \frac{7}{2} \end{bmatrix}$$

put the value in eqn ②

$$\Rightarrow -\frac{V_1}{R} = 5I_1 + 2I_2$$

$$\Rightarrow -5I_2 R - 10I_2 = 5I_1$$

$$\Rightarrow I_2 = \frac{-5I_1}{5R} \Rightarrow I_2 = \frac{I_1}{5}$$

put the value of I_2 in eqn ①

$$\Rightarrow V_1 = 5I_1 - 4 \cdot \frac{I_1}{5}$$

$$= 5I_1 - \frac{4I_1}{5}$$

$$= \frac{25I_1 - 4I_1}{5} = \frac{21I_1}{5} \Rightarrow V_1 = \frac{21I_1}{5}$$

$$2I_1 = 5$$

$$I_1 = \frac{V_1}{21} I_2 = 0$$

$$\Rightarrow 5 = \frac{5I_1}{21} \Rightarrow I_1 = 5$$

$$\text{therefore } I_2 = \frac{V_1}{I_2} = 0$$

$$\Rightarrow 4 = \frac{25}{I_2} \Rightarrow I_2 = \frac{25}{4}$$


put the value of I_1 and I_2 in eqn ③

$$V_2 = 5I_1 + 10I_2$$

$$\Rightarrow V_2 = 5 \cdot 5 + 10 \cdot \frac{25}{4}$$


$$= \frac{100 + 250}{4} = \frac{350}{4} \text{ volt}$$

$$\boxed{V_2 = \frac{175}{2}}$$

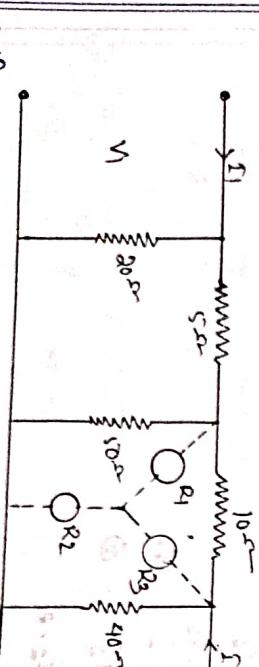


$$R_2 = \frac{50 \times 40}{50+10+40} = \frac{200}{100} = 20 \Omega$$
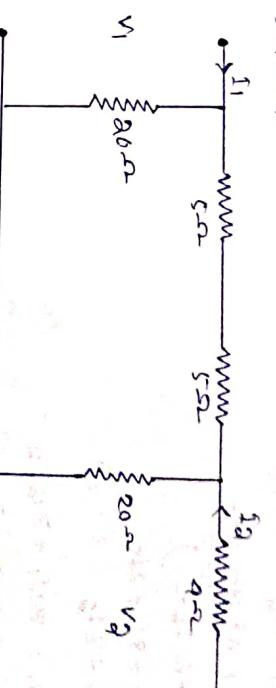
$$R_3 = \frac{10 \times 40}{50+10+40} = \frac{400}{100} = 4 \Omega$$



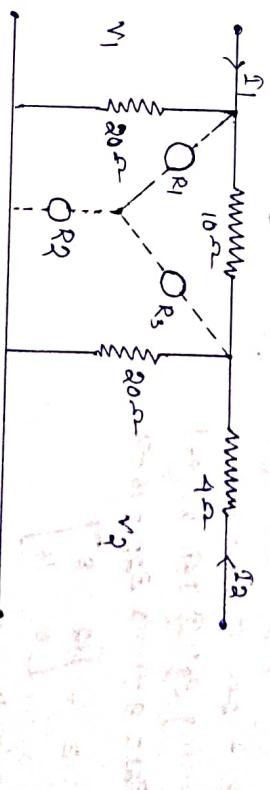5 ohm & 5 ohm are connected in series, so $5+5=10 \Omega$




$$R_1 = \frac{20 \times 10}{20+10+20} = \frac{200}{50} = 40 \Omega$$

$$R_2 = \frac{20 \times 20}{20+10+20} = \frac{400}{50} = 8 \Omega$$


$$R_3 = \frac{20 \times 10}{20+10+20} = \frac{200}{50} = 4 \Omega$$

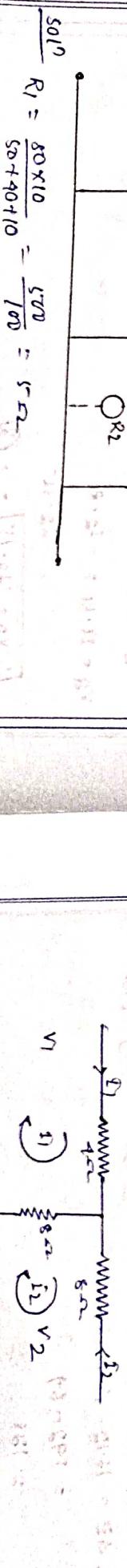4 ohm & 4 ohm are connected in series, so $4+4=8 \Omega$



$$\text{SOL} R_1 = \frac{50 \times 10}{50+40+10} = \frac{500}{100} = 5 \Omega$$

2

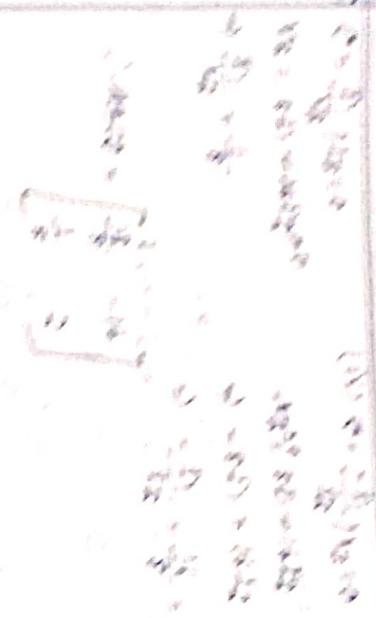

卷之三

卷之三

卷之三

行 14

卷之三

卷之三

卷之三

卷之三

Ottakr. 20. 22

卷之三

卷之三

卷之三

卷之三

Filters

- ⇒ A filter blocks unwanted signals or noise signals and passes wanted or desired signals.
- ⇒ A filter is basically frequency selective network that allows signals of a particular band of frequencies and rejects or attenuates signals of other frequency.
- ⇒ Filter networks are widely used in communication systems to separate various voice channels in carrier frequency to telephone circuit.

They are classified into four common types:-


- (i) Low-Pass Filter (LPF)
- (ii) High-Pass Filter (HPF)
- (iii) Bandpass Filter (BPF)
- (iv) Band stop or Band elimination filter (BSF)

Low-Pass Filter (LPF):-

- ⇒ An LPF passes through low frequency signal and blocks or attenuates signals that have frequencies above selected cut-off frequency (f_c)

Gain

$$\alpha = \frac{V_o}{V_i}$$

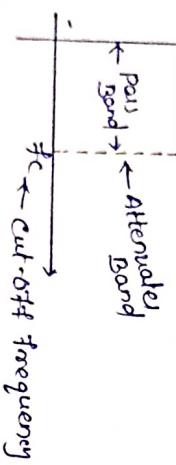

High-Pass Filter (HPF):-

- ⇒ A HPF network will pass only those input signals whose frequencies are above the selected cut-off frequency and attenuates all frequencies below a selected cut-off frequency.


Band Pass Filter (BPF):-

- ⇒ A BPF network passes frequencies between two selected cut-off frequencies and attenuates all other frequencies.


Band Stop Filter (BSF):-

- ⇒ A BSF always passes all frequencies lying outside a range while it attenuates all frequencies below the two selected frequency.

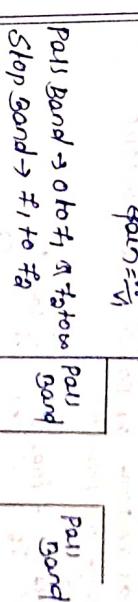It is also called Band elimination filter.



$$\text{Gain} = \frac{V_o}{V_i}$$

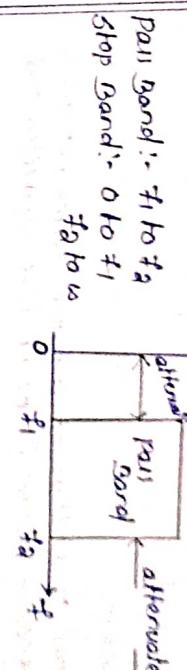

Parameters of a filter:-


There are four important parameters that are necessary to analyze the performance of a filter network.

- (1) Propagation Constant (γ)
- (2) Attenuation Constant (α)
- (3) Phase shift constant (β)
- (4) Characteristic Constant (Z_0)

Propagation Constant (γ):-

- ⇒ For any two-port network terminated by characteristic impedance Z_0 ,
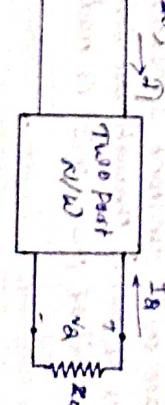
$$\frac{I_1}{I_2} = \frac{V_1}{V_2} = e^{\gamma l} \quad \text{where } l \text{ is length of the line}$$



Band Pass Filter (BPF):

- ⇒ A BPF always passes frequencies between two selected cut-off frequencies and attenuates all other frequencies.

where γ is known as propagation constant.

Propagation constant determines the propagation performance of any two-point network.

$$\gamma = \alpha + j\beta$$

Where α is real part of γ and β is imaginary part of γ and is known as phase constant.

(3) **Attenuation Constant (α):-**

Whenever a signal passes through a passive filter network, it gets attenuated, because passive component like capacitor and inductor consume some of the signal energy.

The attenuation constant determines the attenuation of the signal when it passes through the filter.

Attenuation can be expressed in decibels or nepers.

Decibel:- It is defined as the natural log of the ratio of input current or voltage or power to the output current or voltage or power.

$$\text{Decibel(DB)} = \log_{10} \frac{I_1}{I_2} = \log_{10} \frac{V_1}{V_2} = \log_{10} \frac{P_1}{P_2}$$

Decibel :- It is defined as the ten times the common log of the ratio of input current/voltage/power and output current/voltage/power.

$$D = 20 \log_{10} \frac{I_1}{I_2} = 20 \log_{10} \frac{V_1}{V_2} = 20 \log_{10} \frac{P_1}{P_2}$$

Relation Between Nepers and Decibel :-

Attenuation in Nepers = Attenuation in Decibels

$$8.686$$

Phase shift constant (β):- = 0.115 \times Attenuation in decibel.

When the signal passes through the filter, it gets some shift in phase.

Phase shift constant signifies the phase shift in the signal when it passes through the filter.

The unit of phase shift is radians or degrees.

Characteristic Impedance (z_{c0}):-

Characteristic Impedance is the image impedance of a two-port network.

For symmetrical network, the image impedance of the port is equal to the image impedance of port z_{2-2} . They are equal to the characteristic impedance z .

Inductor pass through DC (Low Frequency) and Block the AC (High Frequency).

Capacitor is passes through AC (High Frequency) and Block the DC (Low Frequency).

Analysis of π -Network:-

$$Z_{OC} = \frac{Z_1 + Z_2}{\alpha}$$

$$Z_{SC} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$\bar{Z}_{OT} = \sqrt{Z_{OC} Z_{SC}} = \sqrt{\frac{Z_1}{\alpha} + Z_2}$$

(Characteristics Impedance)

$$\alpha = 2 \cosh^{-1} \sqrt{\frac{Z_1}{Z_2}}$$

$$\beta = 2 \sin^{-1} \sqrt{\frac{Z_1}{Z_2}}$$

$$8.686$$

$Z_1 + 4Z_2 = 0$ equation to obtain cutoff frequency.

Analysis of π -Network:-

$$Z_{OT} = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$\sqrt{\frac{Z_1}{\alpha} + Z_2}$$

$$Z_{OT} = \sqrt{Z_{OC} \cdot Z_{SC}}$$

$$Y = \frac{2}{Z_{OT}} \sqrt{\frac{Z_1}{Z_2}}$$


$$\alpha = 2 \cosh^{-1} \sqrt{\frac{Z_1}{Z_2}}$$

$$\beta = 2 \sin^{-1} \sqrt{\frac{Z_1}{Z_2}}$$

$$B = 2 \sin^{-1} \sqrt{\frac{Z_1}{Z_2}}$$

$$\boxed{1} \quad \boxed{2}$$

$$Z_1 + 4Z_2 = 0$$

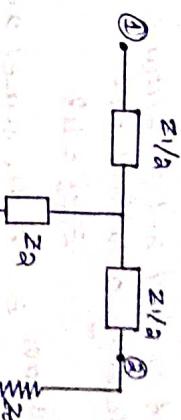

Classification of filters:-

Filters may be classified to be

- Constant u -type or prototype filter
- m -derived filter

Constant u -type or prototype filter:-

A constant u -type filter is a filter that satisfies the following relationship:-

$$Z_1 Z_2 = u^2$$

where, Z_1 is the series arm impedance

Z_2 is the shunt arm impedance

u = Design impedance or nominal impedance or zero

Characteristic impedance.

Constant u -type filter can be of π -type or η -type.

Constant u -type filters may be of low pass type and High pass type, band pass type or band-stop type.

Constant u -type low pass filter (LPF):-

In LPF, the series element is inductor and shunt element is capacitor. T and π selection for constant u -type LPF.



(Fig:- Constant u -type filter)

Resigned Impedance (u):-

Total series Impedance $Z_1 = j\omega L$

Total shunt Impedance $Z_2 = \frac{1}{j\omega C}$

For constant u -type filters, $Z_1 Z_2 = u^2$

$$\frac{L}{C} = u^2$$

$$\Rightarrow u = \sqrt{\frac{1}{C}}$$

$\Rightarrow K = \sqrt{\frac{L}{C}}$ This is the expression that will be used in design of constant u LPF.

Some value of constant u -type LPF:-

$$\text{Design Impedance} :- u = \sqrt{\frac{L}{C}}$$

$$\text{Design parameters} :- L = \frac{u}{\pi f_c} \quad C = \frac{1}{u \pi f_c}$$

$$\text{Cut-off frequency} = f_c = \frac{1}{\pi \sqrt{LC}}$$

$$\text{Attenuation} :- \alpha = 2 \cosh^{-1} \left(\frac{f}{f_c} \right) \text{ in stop band}$$

$$= 0 \text{ in pass band}$$

$$\text{phase constant} = (\beta) = 2 \sin^{-1} \left(\frac{f}{f_c} \right) \text{ in pass band}$$

$$= \pi \text{ in stop band}$$

Characteristics Impedance:-

$$Z_{\text{tot}} = u \sqrt{1 - \left(\frac{f}{f_c} \right)^2}$$


$$Z_{\text{on}} = \frac{u}{\sqrt{1 - \left(\frac{f}{f_c} \right)^2}}$$

Constant u -type High-pass filter (HPF):-

In an HPF, the series element is a capacitor and the shunt arm element is an inductor that is.

$$Z_1 = \frac{1}{j\omega C} \text{ and } Z_2 = j\omega L$$

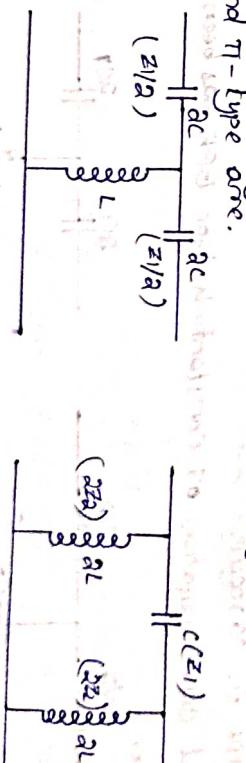The cut configuration of constant u -type HPF, both T -type and π -type one.



Same parameters value of u -type HPF:-

$$\text{Design Impedance} = u = \sqrt{\frac{L}{C}}$$

$$\text{Cut-off frequency} = f_c = \frac{1}{\pi \sqrt{LC}}$$

③ Design parameter :- $\ell = \frac{u}{\omega_0^2 C}$

$$C = \frac{1}{\omega_0^2 \ell^2}$$

④ Attenuation :- $\alpha = 2 \cosh^{-1} \left(\frac{\ell}{2} \right)$ in stop band

$\alpha = 0$ in pass band


⑤ Phase constant :- $\beta = \pi / \ell$ in stop band

$$= 2 \sin^{-1} \left(\frac{\ell}{2} \right) \text{ in pass band}$$

⑥ Characteristics Impedance :- $Z_{0r} = u \sqrt{1 - \left(\frac{\ell}{2} \right)^2}$

$$Z_{0r} = \frac{u}{\sqrt{1 - \left(\frac{\ell}{2} \right)^2}}$$

⑦ Constant π -type band pass filter :-

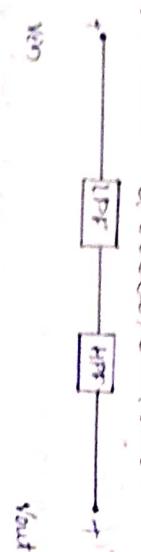

→ A band pass filter can be obtained by connecting a LPF and a HPF in cascade.

→ The chl configuration of constant π -type BPF has been

T-section :-



$\frac{u}{2}$

$$(4) \text{ Attenuation} (\alpha) = \beta \cosh^{-1} \sqrt{\left(\frac{1 - \omega^2}{\omega_0^2} \right)}$$

$$(5) \text{ Phase constant} (\beta) = 2 \sin^{-1} \sqrt{\left(\frac{(1 - \omega^2)}{\omega_0^2} \right)}$$

(6) Characteristics Impedance

$$Z_{0T} = \frac{U}{I} \sqrt{\frac{1 - (1 - \omega^2)}{\omega_0^2 \alpha}}$$

$$Z_{0T} = \frac{U}{I} \sqrt{\frac{(1 - \omega^2)}{\omega_0^2 \alpha}}$$



(7) Design Parameters,

$$C_1 = \frac{U_1 - I_2}{U \cdot 4\pi f_1 f_2}; \quad L_2 = \frac{U(C_1 - C_2)}{4\pi f_1 f_2}$$

$$L_1 = \frac{U}{\pi(C_1 - C_2)}; \quad C_2 = \frac{1}{4\pi f_1 f_2}$$

Constant K-type Band stop filter:-

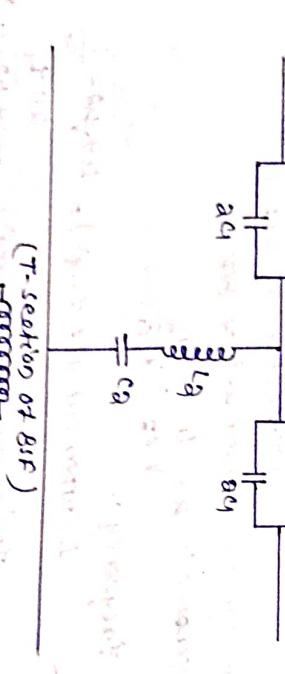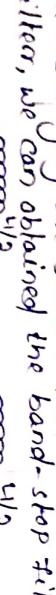By interchanging the series and shunt arms of the band pass filter, we can obtain the band-stop filter.



Some parameter values of constant K-type BPF :-
Design impedance :- $\mu = \sqrt{\frac{U_1}{U_2}} = \sqrt{\frac{U_1}{U_2}}$

(1) Cut-off frequency :-
 f_1 (lower cut off freq) = $\sqrt{\frac{1 + 16\mu^2}{4}}$
 f_2 (upper cut off freq) = $\sqrt{\frac{1 + 16\mu^2}{4\mu^2}}$

Attenuation (α) :-

$$\alpha = 2 \sin^{-1} \sqrt{\frac{\omega_0^2 \mu^2}{\gamma(1 - \omega^2)}}$$

Phase shift (β) :-

$$\beta = 2 \sin^{-1} \sqrt{\frac{\omega_0^2 \mu^2}{\gamma(1 - \omega^2)}}$$

Resonant frequency (ω_0) = $\sqrt{f_1 f_2}$

(6) Characteristics Impedance (Z_{0T}) :-

$$Z_{0T} = \sqrt{\frac{U^2 - \omega_0^2 U^2}{4(1 - \omega_0^2)}}$$

$$Z_{0T} = \frac{U^2}{\omega_0^2 - \frac{\omega_0^2 U^2}{4(1 - \omega_0^2)}}$$

(7) Design Parameters:-

$$L_1 = \frac{U(f_2 - f_1)}{\pi f_1 f_2}; \quad C_1 = \frac{1}{4\pi U f_2 f_1}$$

$$L_2 = \frac{U}{4\pi(f_2 - f_1)}; \quad C_2 = \frac{f_2 - f_1}{4\pi U f_2 f_1}$$

Example-1 Design a T-section having a cut-off frequency of 10MHz to operate with a terminated load resistance of $50\text{m}\Omega$.

Solution It is given that $u = \sqrt{\frac{L}{C}} = 50\text{MHz}$

$$u = \sqrt{\frac{L}{C}} = 50\text{MHz}$$

$$L = \frac{u^2}{\pi^2} = \frac{50^2}{\pi^2 \times 10^9} = 79.6 \text{ mH}$$

$$C = \frac{1}{\pi^2 L} = \frac{1}{\pi^2 \times 79.6 \times 10^{-9}} = 0.512 \text{ pF}$$

$$L = 79.6 \text{ mH}$$

$$L = 79.6 \text{ mH}$$

$$C = 0.512 \text{ pF}$$

$$C = 0.512 \text{ pF}$$

Example-2 Design a T-section having a cut-off frequency of 50Hz with a load resistance of 600Ω .

Solution Given $R_L = u = 600\Omega$ & $\omega_c = 2000\text{Hz}$

$$L = \frac{u^2}{\pi^2 R_L} = \frac{600^2}{\pi^2 \times 600} = 17.74 \text{ mH}$$

$$C = \frac{1}{\pi^2 L} = \frac{1}{\pi^2 \times 17.74 \times 10^{-9}} = 0.133 \text{ pF}$$

$$C = 0.133 \text{ pF}$$

Example-3 Design a band-pass filter having a design impedance of 500Ω and cut-off frequencies 1MHz and 10MHz .

Solution Given

$$u = 500\Omega, f_1 = 1000\text{Hz}, f_2 = 1000\text{MHz}$$

$$L_1 = \frac{u}{\pi(f_2 - f_1)} = \frac{500}{\pi \times 1000 \times 1000} = \frac{5.55}{\pi} \text{ mH} = 16.68 \text{ mH}$$

$$C_1 = \frac{f_2 - f_1}{4\pi u^2 f_2} = \frac{900}{4\pi \times 500 \times 1000 \times 1000} = 0.193 \text{ pF}$$

$$L_2 = C_1 u^2 = 3.57 \text{ mH}$$

$$C_2 = L_2 / u^2 = 0.070 \text{ mH}$$

Each of the two series arms of the constant u , T-section filter is given by

$$\frac{L_1}{2} = \frac{17.74}{2} = 8.87 \text{ mH}$$

$$2C_1 = 2 \times 0.193 = 0.386 \text{ pF}$$

And the shunt-arm elements of the filter are given by.

$$C_2 = 0.0707 \text{ pF} \text{ & } L_2 = 3.57 \text{ mH}$$

$$C_1 = 0.193 \text{ pF} \text{ & } L_1 = 16.68 \text{ mH}$$

$$\frac{C_2}{2} = \frac{0.0707}{2} = 0.0352 \text{ pF}$$

$$2L_2 = 2 \times 0.0707 = 0.1414 \text{ mH}$$

$$C = 0.193 \text{ pF}$$

Example-4 Design a band-stop filter having a design impedance of 600Ω and cut-off frequencies $f_1 = 4\text{MHz}$ & $f_2 = 6\text{MHz}$.

Solution Given

$$u = 600\Omega, f_1 = 4000\text{Hz}, f_2 = 6000\text{Hz}$$

$$L_1 = \frac{u}{\pi(f_2 - f_1)} = \frac{600}{\pi \times 2000 \times 600} = 63 \text{ mH}$$

$$C_1 = \frac{1}{4\pi u^2 f_2} = \frac{1}{4\pi \times 600^2 \times 6000} = 0.083 \text{ pF}$$

Poly Phase Circuit

⇒ Poly phase system is a combination of two or more than two voltages having same magnitude and frequency but displaced from each other by an equal electrical angle.

⇒ Poly means → Many (more than one)

$$\begin{aligned} l_2 &= \frac{1}{4\pi(\mu_2 \cdot r)} = \frac{1}{4\pi \times 4000} = 12 \text{ mH} \\ C_2 &= \frac{1}{l_2 \cdot \pi} \left\{ \frac{\mu_2 - r_2}{H_1 H_2} \right\} = \frac{1}{600 \times \pi} \left(\frac{4000}{2000 \times 600} \right) = 0.196 \text{ aef} \end{aligned}$$

each of the two series arms of the constant u_1 , T-section filter

$$\frac{u_1}{2} = \frac{63}{2} = 31.5 \text{ mH}$$

$$2C_1 = 0.033 \times 2 = 0.066 \text{ aef}$$

and shunt arm elements of the u_2 arm:

$$l_2 = 12 \text{ mH}, \quad C_2 = 0.176 \text{ aef}$$

⇒ For the constant u_1 , π -section filter, the series arm to

$$u_1 = 63 \text{ mH}, \quad C_1 = 0.033 \text{ aef}$$

Short arm are

$$2l_2 = 2 \times 12 = 24 \text{ mH}$$

$$\frac{C_2}{2} = \frac{0.176}{2} = 0.088 \text{ aef}.$$

Advantage of 3φ systems:-


⇒ The O/P of 3φ machine generating electricity is more than O/P of a 1φ machine of same size.

⇒ The most commonly used 3φ induction motor are self starting but for 1φ motor, a separate starting winding is required.

⇒ The power factor of 3φ system is better than that of the single phase system.

⇒ Single phase supply can also be obtained from a 3φ system.

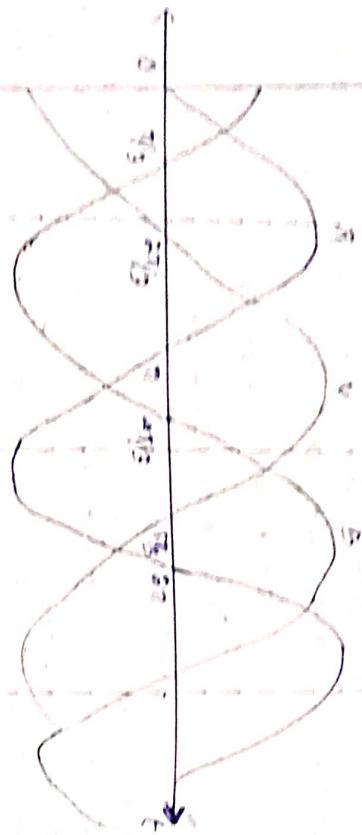⇒ For magnetization of ac to dc, the DC O/P voltage becomes less fluctuating if the number of phases is increased.



(\Rightarrow Three-phase system or balanced voltage)

Phase Sequence:-

\Rightarrow The order in which the maximum value of voltage of each phase occurs is called the phase sequence.

\Rightarrow It can be, $E_1E_2E_3$ or $E_2E_3E_1$

We can write in sinusoidal form,

$$V_{ph} = V_m \sin(\omega t - \phi)$$

Symmetrical system: (or Balanced supply)

\Rightarrow In a Symmetrical system, the magnitude of 3P voltage is the same but there is a time phase difference of 120° between the voltage.

Unbalanced supply:-

\Rightarrow A 3P system is said to be unbalanced when either of the 3P voltage are equal to magnitude or the phase angle between the three phase is not equal to 120° .


Three phase winding connection:-

\Rightarrow A 3P generator will have 3P winding. These phase winding can be connected in two ways,

\Rightarrow Star connection

\Rightarrow Delta connection.

(2) STAR CONNECTION (Y):-

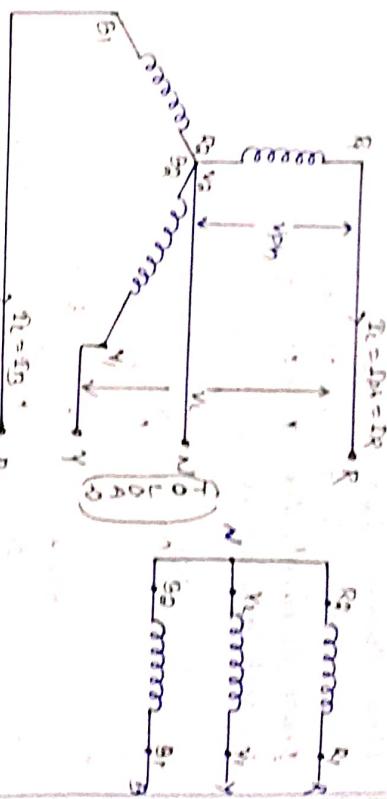

\Rightarrow The star connection formed by connecting the starting or finishing end of all the three winding together. A fifth conductor, that is taken out of the star point is called the neutral point. The remaining three end are brought out for connection to load.

\Rightarrow The current flowing through each line conductor is called line current (I_L).

\Rightarrow In star connection, the line current is also the phase current.

\Rightarrow The voltage across the each phase is called phase voltage (V_{ph}) and voltage across any two line conductor is called line voltage (V_L).

\Rightarrow In balanced three phase load, the sum of their current that is $I_{L1} + I_{L2} + I_{L3}$ will be zero.


\Rightarrow The natural wine connected between the supply neutral point and the load neutral point will carry no current for a balance system.

Considered the balanced star-connected system.

\Rightarrow Suppose the load is inductive therefore current will lag the applied voltage by an angle ϕ .

\Rightarrow In balanced system, the magnitude of current and voltage at each phase will be the same.

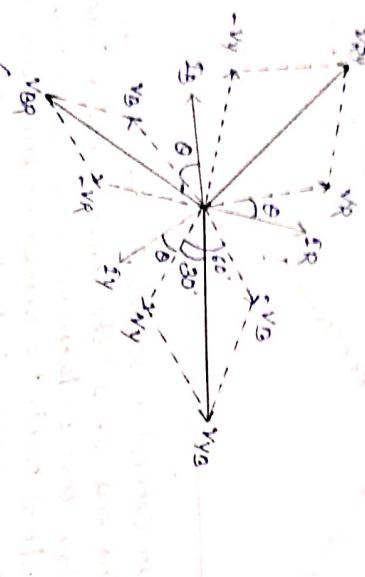Phase voltage: $V_R = V_B - V_A = V_L$
 Line current: $I_L = I_R = I_B = I_A$
 Line voltage: $V_L = V_{RY} = V_{RB} = V_{AB}$
 Power: Current, $I_R = I_B = I_A = I_L$
 In star connection, $I_L = I_R$



(Fig:- Phasor Diagram)

To derive relation between V_L & V_{RY}

$$V_{RY} = V_{RN} + (-V_{RN})$$

$$V_{RB} = V_{RN} + (-V_{RN})$$

$$V_{BR} = V_{BN} + (-V_{BN})$$

From the phasor diagram, the phase angle between phasor V_{RY} & V_R is 60° .

$$V_{RY} = \sqrt{V_R^2 + V_B^2 + 2V_R V_B \cos 60^\circ}$$


$$V_L = V_R = \sqrt{V_{RN}^2 + V_{BN}^2 + 2V_{RN} V_{BN} \cos 60^\circ}$$

$$V_L = V_3 V_{ph}$$

Thus, for the star-connection system, $V_L = V_{RN} + V_{BN}$

$$\begin{aligned} \rightarrow \text{line voltage} &= V_3 \times \text{phase voltage} \\ \rightarrow \text{line current} &= \text{phase current.} \end{aligned}$$

(a) Delta Connection (Δ):-

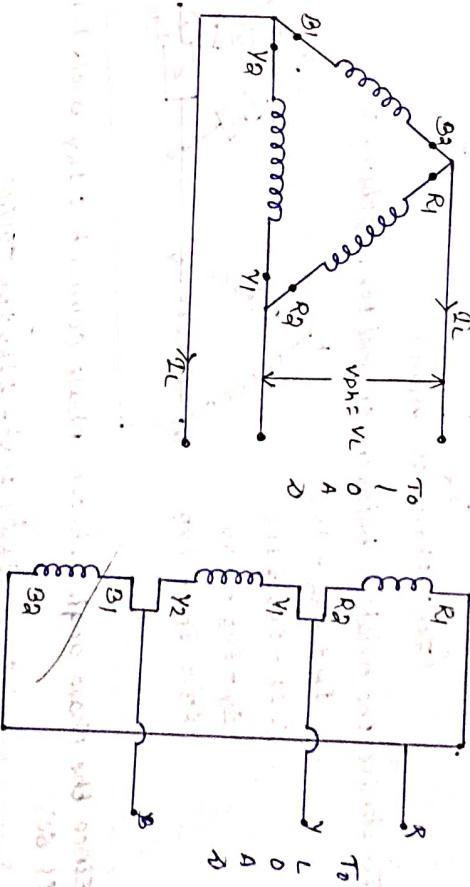

Power:
 Power output per phase = $V_{ph} I_{ph} \cos \phi$
 Total power output = $3 V_{ph} I_{ph} \cos \phi$
 $= 3 \times \frac{V_L}{\sqrt{3}} \times I_L \cos \phi$
 $P = \sqrt{3} V_L I_L \cos \phi$

$$\therefore \text{Power} = \sqrt{3} \times \text{Line voltage} \times \text{Line current} \propto \text{P.F.}$$

- ⇒ The delta connection is formed by connecting the end of one winding is starting end of the other and connections are continued to form a closed loop.
- ⇒ In delta connection, the current flowing through each line conductor is called line current (I_L) and the current flowing through each phase winding is called phase current (I_{ph}).
- ⇒ In delta connection, phase voltage is same as line voltage ($V_R = V_R$)
- ⇒ In balanced delta connection system, the current through the phase is not the same as through the supply line.

$$\text{Line voltage} \Rightarrow V_L = V_{RY} = V_{RB} = V_{AB}$$

$$\text{Line current} \Rightarrow I_L = I_R = I_B = I_A$$

$$\text{Phase voltage} \Rightarrow V_{ph} = V_{RY} = V_{RB} = V_{AB}$$


$$\text{Power} = V_L I_L \cos \phi$$

$$P = V_L I_L \cos \phi$$

$$\text{Power} = \sqrt{3} \times \text{Line voltage} \times \text{Line current} \times \text{P.F.}$$

If per phase power P_h and total power is P_T , then


$$[P_T = 3P_h]$$

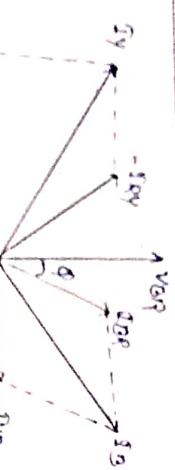

(Fig: phasor diagram)

⇒ To derive the relation between I_R and I_{ph} , applying nec.
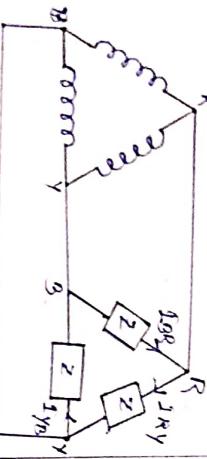
$$\begin{aligned} & I_R + I_{BR} = I_{RY} \\ \therefore & I_R - I_{RY} = I_{BR} \\ I_3 &= I_{BR} - I_{RY} \end{aligned}$$



Since the phase angle between phase current I_{RY} and I_{BR} is 60° .

$$\therefore I_R = \sqrt{I_{RY}^2 + I_{BR}^2 + 2I_{RY}I_{BR} \cos 60^\circ}$$

$$I_R = I_c = \sqrt{I_{BR}^2 + I_{RY}^2 + 2I_{RY}I_{BR} \cos 60^\circ}$$

$$I_R = \sqrt{3I_{ph}^2 + I_{ph}^2}$$

$$[I_R = \sqrt{3}I_{ph}]$$

⇒ Star delta connected 3-p system.

⇒ Line current = $\sqrt{3}$ phase current

⇒ Line voltage = phase voltage.



Power: Power per phase = $V_{ph}I_{ph} \cos \phi$

Total power output = $3V_{ph}I_{ph} \cos \phi$

$$[P = \sqrt{3}V_{ph}I_{ph} \cos \phi]$$

Measurement of Power in Three-phase circuit:-
Two wattmeter method:-

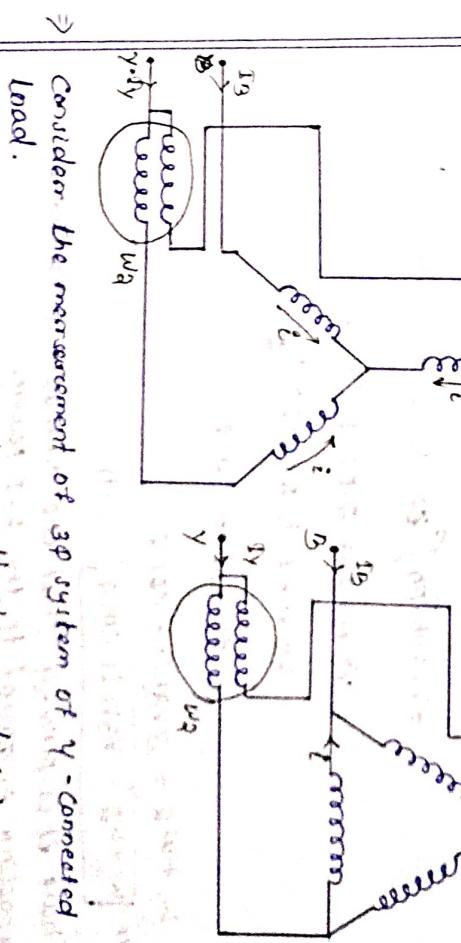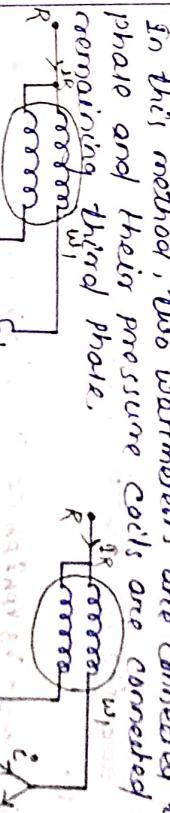In this method, two wattmeters are connected to two phase and their pressure coils one connected to the remaining third phase.



Consider the measurement of 3-p system of Y-connected load.

Let w_1, w_2 be the two wattmeter reading.

The current flowing through the current coil of wattmeter w_1 is I_R . The voltage appearing across it pressure coil is V_{RY} . The wattmeter reading w_1 will be equal to $w_1 = V_{RY}I_R \cos \phi$. The angle between V_{RY} and I_R . Similarly the wattmeter reading w_2 will be equal to $w_2 = V_{YB}I_B \cos \phi$. The angle between V_{YB} and I_B .



V_{1A}

w_1

V_{3A}

w_2

V_{2A}

$$W_1 = V_{1A} \sin \cos(30 - \phi) = V_3 V_{ph} I_{ph} \cos(30 - \phi) = V_{1A} \cos(30 - \phi)$$

$$W_2 = V_{3A} \sin \cos(30 + \phi) = V_3 V_{ph} I_{ph} \cos(30 + \phi) = V_{3A} \cos(30 + \phi)$$

Let we add the two wattmeter readings that is $w_1 + w_2$.

$$w_1 + w_2 = V_3 V_{ph} I_{ph} \cos(30 - \phi) + V_3 V_{ph} I_{ph} \cos(30 + \phi)$$

$$= V_3 V_{ph} I_{ph} \left\{ \cos(30 - \phi) + \cos(30 + \phi) \right\}$$

$$= V_3 V_{ph} I_{ph} 2 \cos \phi \cos 30^\circ$$

$$= 3 V_{ph} I_{ph} \cos \phi$$

$$W_1 + W_2 = 3 V_{ph} I_{ph} \cos \phi$$

Thus it is proved that the sum of the wattmeter readings is equal to the 3-ph power.

Now when the two wattmeter readings are subtracted from each other, we obtained.

$$\Rightarrow W_1 - W_2 = V_3 V_{ph} I_{ph} \left\{ \cos(30 - \phi) - \cos(30 + \phi) \right\}$$

$$\Rightarrow W_1 - W_2 = V_3 V_{ph} I_{ph} 2 \sin \phi \cdot \sin 30^\circ$$

$$\Rightarrow V_3 (W_1 - W_2) = V_3 \times V_3 I_{ph} \cdot I_{ph} \cdot 2 \sin \phi \cdot \sin 30^\circ$$


$$\Rightarrow \boxed{V_3 (W_1 - W_2) = V_3^2 I_{ph} \sin \phi} \quad - (ii)$$

$$\text{Dividing eqn (i) by (ii)}$$

$$\frac{V_3 (W_1 + W_2)}{V_3 (W_1 - W_2)} = \frac{V_3 V_{ph} I_{ph} \cos \phi}{V_3^2 I_{ph} \sin \phi} = \tan^{-1} \frac{W_1 + W_2}{W_1 - W_2}$$

$$\Rightarrow \phi = \tan^{-1} \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} \rightarrow \text{Power factor}$$

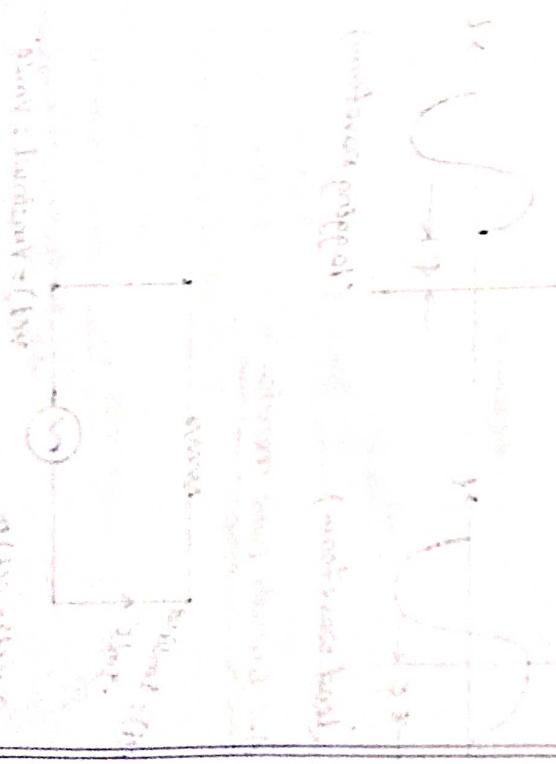From two wattmeter reading we can calculate the total active and reactive power and the P.F of the cat.




Another method to find power factor

Power factor = $\frac{\text{Actual Power}}{\text{Apparent Power}}$

AC Circuit

The sin wave is represented by the equation:

$$v(t) = V_m \sin(\omega t)$$

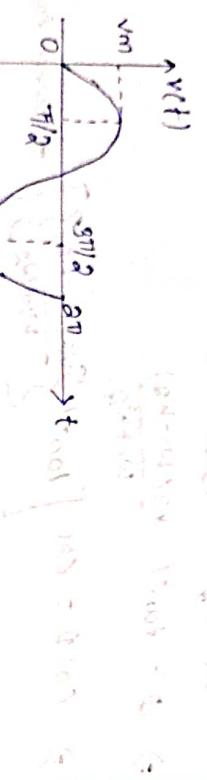

(Reference sine wave form)


(i) If a sin wave is shifted to the left of the reference wave by a certain angle ϕ .

$$v(t) = V_m \sin(\omega t + \phi)$$

(ii) If a sine wave is shifted to the right of the reference wave by a certain angle ϕ .

$$v(t) = V_m \sin(\omega t - \phi)$$

A.C through pure resistor

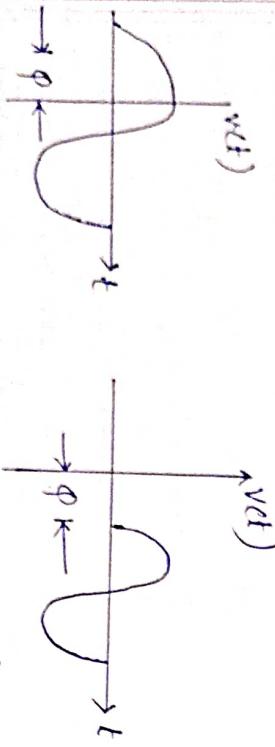

(lead waveform)

(lagging waveform)

④ A.C through pure resistor!

$$i(t) = \frac{V_m}{R} \sin(\omega t)$$


$$\Rightarrow v(t) = i(t)R$$

$$\Rightarrow V_m = I_m R$$

$$\Rightarrow [V_m = I_m R]$$

$$\text{on } V_m^2 = I_m^2 R$$

⇒ Phasor Diagram:-

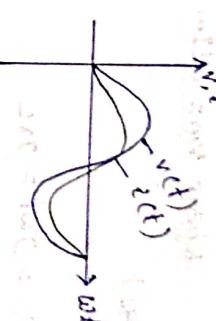


(lead waveform)

In case of resistor

$$Z = \frac{V_m}{I_m}$$

[$Z = R$]

② Ac through pure Inductor:-

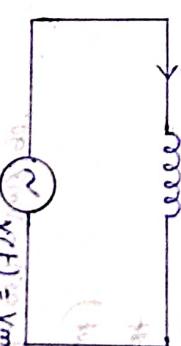

(lagging waveform)

$$\Rightarrow V = L \frac{di}{dt}$$

$$\Rightarrow \theta = i(t) = I_m \sin(\omega t) = I_m \cos(90^\circ)$$

$$v(t) = L \frac{d}{dt} (I_m \sin(\omega t))$$

$$v(t) = L \omega I_m \cos(\omega t)$$

$$v(t) = V_m \cos(\omega t)$$

$$v(t) = V_m \cos(\omega t + 90^\circ)$$

where,

$$V_m = L \omega I_m = X_l I_m$$

∴ In a pure inductor the voltage V_m and current are out of phase.

and current lags behind the voltage by 90° :



⇒ There is no phase difference between these two waveforms.


⇒ Impedance :-

In case of resistor

$$Z = \frac{V_m}{I_m}$$

[$Z = R$]

③ Ac through pure capacitor:-

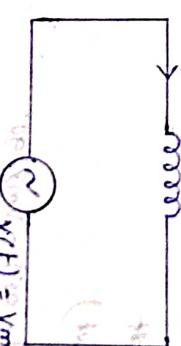

(lagging waveform)

$$\Rightarrow V = \frac{Q}{C}$$

$$\Rightarrow \theta = i(t) = Q/C = I_m \cos(90^\circ)$$

$$v(t) = C \frac{d}{dt} (I_m \cos(90^\circ))$$

$$v(t) = V_m \sin(\omega t)$$

$$v(t) = V_m \sin(\omega t)$$

$$v(t) = V_m \sin(\omega t + 90^\circ)$$

∴ In a pure capacitor the voltage V_m and current are out of phase.

and current leads the voltage by 90° :



Impedance :-

$$Z = \frac{V_m \sin(\omega t + 90^\circ)}{I_m \sin \omega t}$$

$$Z = I_m \omega L \sin(\omega t + 90^\circ)$$

$$Z = \omega L I_m \sin 90^\circ / I_m \cos 90^\circ = \omega L = j\omega L$$

(3) A.c through a pure capacitor :-

AC through a pure capacitor :- voltage across capacitor is $V_m \sin(\omega t - 90^\circ)$



$$\Rightarrow V(t) = V_m \sin(\omega t - 90^\circ)$$

$$\Rightarrow i(t) = \frac{1}{jC} \int V_m \sin(\omega t - 90^\circ) dt$$

$$\Rightarrow V(t) = \frac{1}{C} \int I_m \sin(\omega t) dt$$

$$\Rightarrow V(t) = \frac{1}{C} I_m \sin(\omega t - 90^\circ)$$

$$V(t) = \frac{I_m}{\omega C} \sin(\omega t - 90^\circ) = V_m \sin(\omega t - 90^\circ)$$


$$\text{where, } V_m = \frac{I_m}{\omega C}$$

$$Z = \frac{V_m \angle -90^\circ}{I_m \angle 0^\circ} = \frac{-j}{\omega C}$$

$$Z = \frac{-j}{\omega C}$$


$\therefore Z = \frac{1}{j\omega C} = jX_C$ is called capacitive reactance.

phasor diagram :-

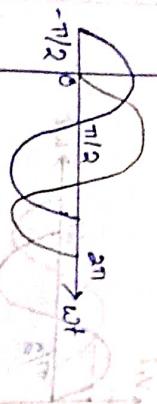

→ In a pure capacitor, the current leads the voltage by 90° .

R-L Series circuit :-

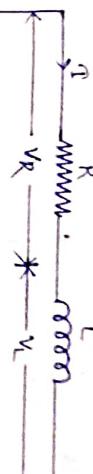

$$[V = V_R + jV_L]$$

• Complex phasor voltage

$$\text{In magnitude, } |V| = \sqrt{V_R^2 + V_L^2}$$

$$\text{In angle, } \angle V = \tan^{-1}\left(\frac{V_L}{V_R}\right)$$

From complex phasor voltage

$$\Rightarrow V = V_R + jV_L$$

$$\Rightarrow V = j(R + j\omega L)$$

$$\Rightarrow \frac{V}{j} = R + j\omega L$$

$$\Rightarrow Z = R + j\omega L$$

$$\Rightarrow |Z| = \sqrt{R^2 + (\omega L)^2}$$


$$\Rightarrow \angle Z = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

Power factor :-

$$\cos \phi = \frac{V_R}{V}$$

Impedance triangle for R-L circuit
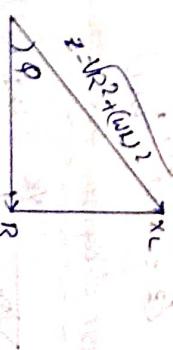
$$\Rightarrow \cos \phi = \frac{R}{\sqrt{R^2 + (\omega L)^2}}$$



$$Z \cos \phi = R$$

$$\Rightarrow \sin \phi = \frac{\omega L}{Z}$$

$$\Rightarrow \tan \phi = \frac{\omega L}{R}$$

$$\Rightarrow \phi = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

(a) Series R-C circuit



Complex phasor voltage given by,

$$\Rightarrow V = V_R - jV_C$$

$$|V| = \sqrt{V_R^2 + V_C^2}$$

$$\angle Z = \tan^{-1} \left[-\frac{V_C}{V_R} \right]$$

From complex phasor voltage,

$$\Rightarrow V = V_R - jV_{XC}$$

$$\Rightarrow V = IR - jIX_C$$

$$\Rightarrow \frac{V}{I} = R - jX_C$$


$$\Rightarrow Z = R - jX_C$$

$$\Rightarrow Z = R - j/X_C$$

$$\Rightarrow |Z| = \sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}$$

$$\angle Z = \tan^{-1} \left[-\frac{1}{\omega C} \right] \quad (X_C = \frac{1}{\omega C})$$

Phasor diagram for series R-C circuit :-

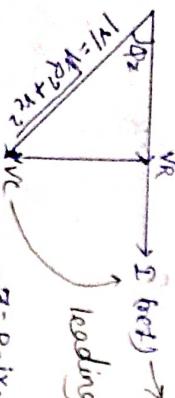

$\phi_2 = 0^\circ$

$\phi_V - \phi_I = 0$

$\phi_I > \phi_V$ reading P.F.

Impedance Triangle !-



$$|Z| = \sqrt{R^2 + X_C^2}$$


Power factor:-

$$\cos \phi = \frac{V_R}{V}$$

$$\cos \phi = \frac{I_R}{I_Z}$$

Series R-C Network :-

Parallel RL Network :-

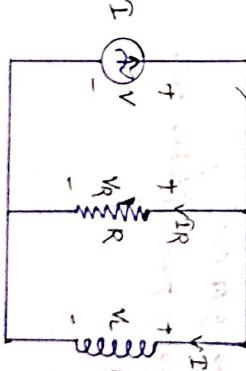

Complex phasor current is
given by

$$I = I_R - jI_L$$

$$|I| = \sqrt{I_R^2 + I_L^2}$$

$$\angle I = \tan^{-1} \left[-\frac{I_L}{I_R} \right]$$

$$\angle I = -\tan^{-1} \left[\frac{I_L}{I_R} \right]$$

$$\phi_R = -\tan^{-1} \left[\frac{I_L}{I_R} \right] = -\tan^{-1} \frac{L}{R}$$

$$Z = R - jX_L$$

$$\phi_2 = -\phi_V$$

$$\phi_2 = \frac{\phi_V}{\phi_I}$$

$$\phi_2 = \phi_R - \phi_V$$

$$V_R = V_L = V \text{ (not voltage)}$$

$$\Rightarrow I = \frac{V}{R} + j\frac{V}{X_L}$$

$$\Rightarrow \frac{I}{V} = \frac{1}{R} + j\frac{1}{X_L}$$

$$\Rightarrow Y = G - jB \quad [G = \frac{1}{R}, B = \frac{1}{X_L}]$$

$$|Y| = \frac{1}{R} + \frac{1}{X_L}$$

$$|Y| = \sqrt{\frac{1}{R^2} + \frac{1}{X_L^2}}$$

$$\delta Y = \phi_Y = \tan^{-1} \left[\frac{1}{R X_L} \right]$$

Phasor diagram:-

Resultant current
Resultant voltage
Current
Voltage

lagging $\rightarrow \delta \phi$
(Fig:- lagging p.f cut)

Parallel R circuit is reknowned also lagging power factor cut.

Power factor :-


$$\cos \phi = \frac{P_R}{V} = P.F$$

$$\cos \phi = \frac{V_R}{V} = \frac{R}{Z}$$

$$Z = (R + jX_L)$$

$$P = \frac{V^2}{Z} = \frac{V^2 R}{R^2 + X_L^2}$$

$$[\cos \phi = \frac{1}{Z}]$$

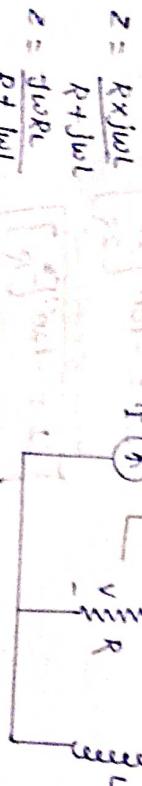


$$\cos \phi = \frac{1}{Z} = \frac{R}{\sqrt{R^2 + X_C^2}}$$

$$\cos \phi = \frac{1}{Z} = \frac{R}{\sqrt{R^2 + \omega^2 C^2}}$$

$$\cos \phi = \frac{P_R}{\sqrt{P_R^2 + Q^2}} = \frac{1}{\sqrt{R^2 + X_C^2}}$$

with parallel R-C circuit :-

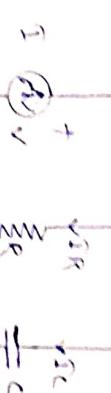


Complex phasor current I is given by

$$I = I_R + jI_C \dots \text{①}$$

$$V = V_R = V_C$$

$$|I| = \sqrt{I_R^2 + I_C^2}$$

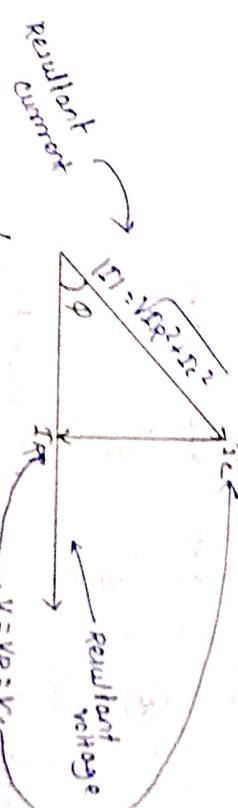

Resultant current
Resultant voltage
(Fig:- leading p.f cut)

Parallel R-C network is reknowned as leading p.f cut like series R-C cut.

$$\Rightarrow I = I_R + jI_C$$

$$\Rightarrow I = \frac{V}{R} + j\frac{V}{X_C}$$

$$\Rightarrow \frac{I}{V} = \frac{1}{R} + j\frac{1}{X_C}$$


$$[\text{as } X_C = \frac{1}{\omega C}]$$

$$\Rightarrow Y = \frac{1}{R} + j\frac{1}{\omega C}$$

$$[|Y| = \sqrt{\frac{1}{R^2} + \omega^2 C^2}]$$

$$[\delta Y = \phi_Y = \tan^{-1} (\frac{1}{R \omega C})]$$

$\phi_Y = +ve$
 $P.F = \text{leading}$.

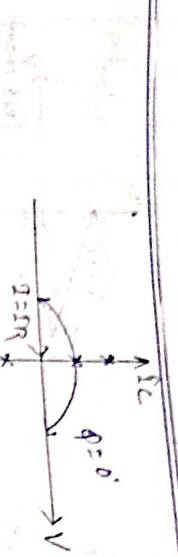

[Fig:- phasor form]

Power factor :-

It describes the direction of resultant current w.r.t. resultant voltage. ($\frac{I}{V}$)

$$\cos \phi = \frac{V_R}{V}$$

$$\cos \phi = \frac{P}{V}$$

$$\cos \phi = \left(\frac{P}{V} \right) R$$



\Rightarrow In case of leading P.F., resultant current will lead from resultant voltage.

\Rightarrow In case of lagging P.F., resultant current will lag from resultant voltage.

In case of lagging P.F., resultant current will lag from resultant voltage.

$$\text{Power} = V I \cos \phi = \text{Active power}$$

$$Q = V I \sin \phi = \text{Reactive power}$$

$$\text{Apparent power} (S) = \text{rms value of voltage} \times \text{rms value of current}$$

$$S = V I T$$

\Rightarrow The apparent power is expressed in volt amperes, that is VA or in kilo-volt amperes is MVA.

$$\text{Then Real or active power} = V I \cos \phi$$

$$P = \text{Apparent power} \times \text{power factor}$$

$$(\text{watt or kilowatt})$$

$$\text{Reactive power} Q = V I \sin \phi (\text{VAR or kilo VAR})$$

$$Q = \text{Apparent power} \times \sin \phi$$


So, there 3 types of powers are related as given in the following:

$$S^2 = P^2 + Q^2$$

$$S = \sqrt{P^2 + Q^2}$$

$$MVA = \sqrt{(MW)^2 + (MVAr)^2}$$

power triangle :-

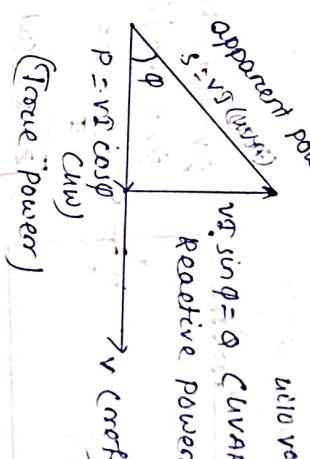

Active power :-

The power which is actually consumed or utilised in an A.C circuit is called True power or Active power.

It is measured in kW or mW.

Reactive power :-

The power which flows back and forth that means it moves in both directions in the circuit or reacts upon itself is called reactive power.

It is measured in kVAR or mVAR.

* RESONANCE *

\Rightarrow Resonance describes the network condition in which inductive and capacitive effects neutralised to each other that mean $X_L = X_C$

(ii) Power factor of the cut will be unity.

(iii) Impedance or admittance of the cut will become resistive.


(iv) Input voltage and input current will be in phase at cut that means angle between input voltage & input current will be zero:

Resonance denotes the condition in which energy stored in conductor and capacitor, the frequency of which, corresponds to the frequency of the applied voltage.

Example of Resonance:

- Series RLC Resonance circuit.
- Parallel RLC Resonance circuit.

Series RLC Resonance circuit:

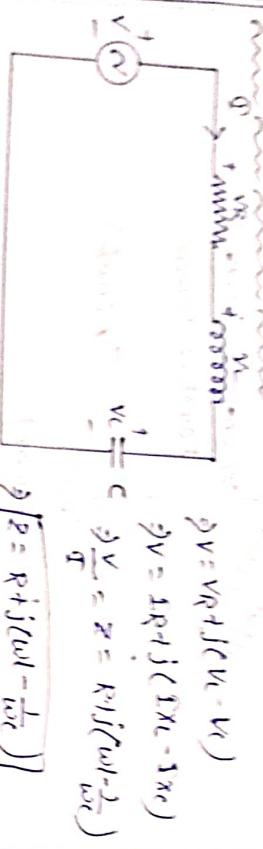

Condition of Resonance:

$$\text{Im}[Z] = 0 \Rightarrow \text{Im}[V] = 0 \Rightarrow \text{Im}[I] = 0$$

$$\text{Im}[V] = 0$$

$$\text{Im}[I] = 0$$

$$\text{Im}[Y] = 0$$

$$V_L - V_C = 0$$

$$V_L = V_C$$

$$IX_L = IC$$

$$X_L = X_C$$

$$WL = \frac{1}{WC}$$

$$\omega_0^2 = \frac{1}{LC}$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

Power factor
Input P.F. = supply P.F. = $P/S = \cos \phi$

$\tan \phi = 1$ and $\theta = 90^\circ$



∴ So, if resonant cut p.f will be unity.

$$P = R^2 j(\omega L - \frac{1}{\omega C})^2$$

$$Z = \sqrt{R^2 + (L\omega - \frac{1}{C\omega})^2}$$

$$Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

Diagram representation:-

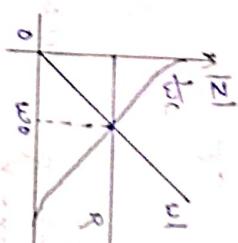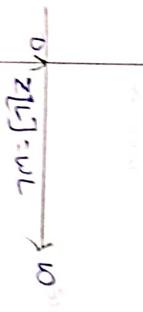

ω	R/LC	$P.F.$
$\omega < \omega_0$	capacitive leading P.F.	
$\omega = \omega_0$	resistive P.F.	
$\omega > \omega_0$	inductive lagging P.F.	

$$(Z^2 = R^2 + (2\omega LC)^2)$$

$$(P.F. = \cos \theta)$$

$$\Rightarrow |P| = \frac{V}{|Z|}$$


$$|P| = \sqrt{\frac{V^2}{R^2 + (\omega L - \frac{1}{\omega C})^2}}$$

$$|I_{\text{max}}| = \omega = \frac{V}{Z_{\text{min}}} = \frac{V}{R}$$

\Rightarrow Quality factor :- (Q factor)
 \Rightarrow Quality factor describes the energy storage capability of Inductor and capacitor in RLC networks.

\Rightarrow High value of quality factor represent high energy storage capability of network.

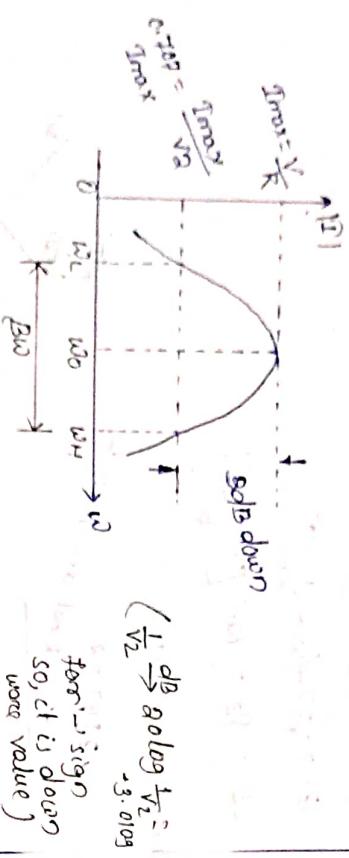
$$Q_{[L]} = 2\pi \times \frac{\text{Energy stored by inductor}}{\text{Energy displaced by resistor per cycle}}$$



$$(\frac{1}{\sqrt{2}} \rightarrow \text{alog } \frac{1}{\sqrt{2}} = 3.090)$$

Resonance:-
Series RLC

①

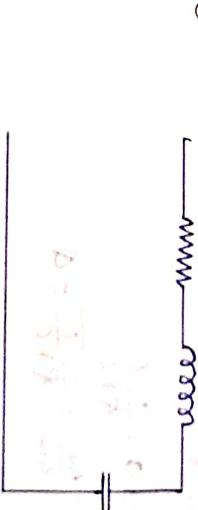

at resonance condition

when, $\omega = \omega_0$

$$V_R = V$$

For Inductor

$$\Rightarrow Q_{[L]} = \frac{V_R \omega}{V} = \frac{V_R}{V}$$

$$\Rightarrow Q_{[L]} = \frac{\omega_0 L}{R} = \frac{\omega_0}{R}$$

$$\text{where, } \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow Q_{[L]} = \frac{L}{R} \times \omega_0 = \frac{L}{R} \times \frac{1}{\sqrt{LC}} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

for capacitor

$$\Rightarrow Q_{[C]} = \frac{\omega_0}{R} = \frac{1}{\omega_0 C} = \frac{V_R}{V}$$

at $\omega = \omega_0$

$$V_R = V$$

$$Q_{[C]} = \frac{1}{R} \sqrt{\frac{C}{L}}$$

$$Q_{[C]} = \frac{1}{R} \sqrt{\frac{C}{L}}$$

$$Q_{[C]} = \frac{1}{R} \sqrt{\frac{C}{L}}$$

$$Q[R] = \frac{V_R}{V} = \frac{V_R}{V_R + V_C}$$

$$Q[C] = \frac{1}{P_{RC}} = \frac{1}{P_{RC}C}$$

$$Q[L] = \frac{1}{P_{RC}L} = \frac{1}{P_{RC}} \cdot \frac{1}{V_{RL}} = \frac{1}{P_{RC}} \cdot \frac{\sqrt{L}}{2}$$

$$Q[R] = \frac{1}{R} \sqrt{\frac{L}{C}}$$

(For resonance condition)

Quality factor of series RLC

$$Q_{series} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$Q_{series} = \pm Q_{R, L, C}$$

Basic result of series RLC resonance circuit

$$(i) \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$

$$(ii) Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$(iii) g_0 = \frac{R}{L} \text{ rad/sec}$$

$$(iv) \frac{\omega_0}{g_0} = \frac{1}{R} \sqrt{\frac{L}{C}} = Q$$

$$\frac{\omega}{g_0} = Q$$


Resonant frequency = quality factor

Example

$$g_0 \omega = 10 \text{ mHz}, f_0 = 1 \text{ mHz}$$

$$Q, \frac{\omega_0}{g_0} = \frac{f_0}{g_0 \omega_0} = \frac{1 \times 10^4}{10 \times 10^6} = 0.1$$

Parallel RLC Resonance circuit

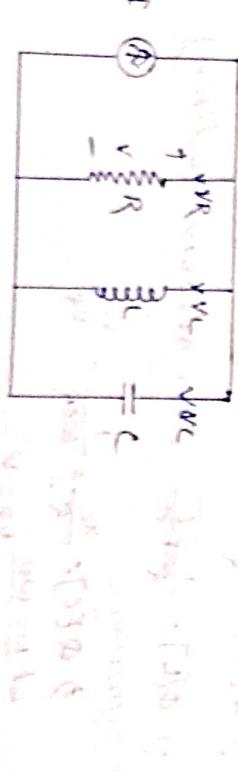

$$\Rightarrow P_T = I_R R + j(I_R - I_L) = \dots \quad (1)$$

$$\frac{T}{V} = \frac{1}{R} + j\left(\frac{1}{LC} - \frac{1}{\omega L}\right)$$

$$\gamma = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$

Condition of Resonance

$$\operatorname{Im}[T] = 0$$

$$\Rightarrow T_C = T_L$$

$$\Rightarrow \frac{V}{X_C} = \frac{V}{X_L}$$

$$X_C = X_L$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$


$$(or) \operatorname{Im}[Y] = 0$$

$$\omega_0 C = \frac{1}{\omega_0 L} = 0$$

$$\omega_0^2 = \frac{1}{LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$

Diagram Representation :-

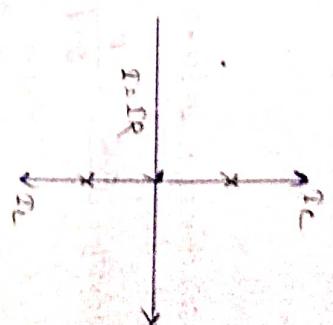

$$\omega_0$$

CHAPTER

TRANSIENTS

Steady state response is concerned as permanent response because this response doesn't varies with time.

Transient response is referred as temporary response because these response varies with time.

ω	R/LC	P.F.
Inductance	L	lagging P.F.
Resistance	R	UPF
Capacitance	C	Leading P.F.

Selectivity \Rightarrow

Selectivity is defined as the ratio of bandwidth to resonant frequency.

$$\text{Selectivity} = \frac{B.W}{f_0} = \frac{f_u - f_l}{2\pi f_0}$$

Quality factor (Q factor) :-

It is defined as the ratio of $2\pi f_0$ maximum energy stored to energy dissipated per cycle.

$$Q \text{ factor} = \frac{2\pi f_0 \frac{1}{2} L I^2}{I^2 R T}$$

$$= \frac{2\pi f_0^2}{R T} = \frac{2\pi f_0^2}{T^2 R T} = \frac{2\pi f_0^2}{T^2 R}$$

$$\text{Quality factor} = \frac{2\pi f_0^2}{R}$$

Quality factor defined as the reciprocal of P.F.

$$Q \text{ factor} = \frac{1}{P.F}$$

It is reciprocal of selectivity

Q factor or magnification factor = $\frac{\text{Voltage across Inductor}}{\text{Voltage across capacitor}}$


$$= \frac{L \frac{dI}{dt}}{\frac{1}{C} \frac{dV}{dt}} = \frac{L \frac{dI}{dt}}{\frac{dV}{C dt}} = \frac{L dI}{C dV} = \frac{L}{C} = \text{Quality factor.}$$

$$Q \text{ factor} = \frac{\text{Voltage across Capacitor}}{\text{Voltage across Resistor}} = \frac{C \frac{dV}{dt}}{R} = \frac{C}{R} \cdot \frac{dV}{dt}$$

$$Q \text{ factor} = \frac{1}{R C R}$$

$$\text{Response} = Q^2 = \frac{1}{C^2} \times \frac{1}{R^2} \times \frac{1}{L^2} \times \frac{1}{R^2 C^2} \Rightarrow Q^2 = \frac{1}{R^2 C^2} \Rightarrow Q = \sqrt{\frac{1}{R^2 C^2}} \Rightarrow Q = \frac{1}{R C}$$

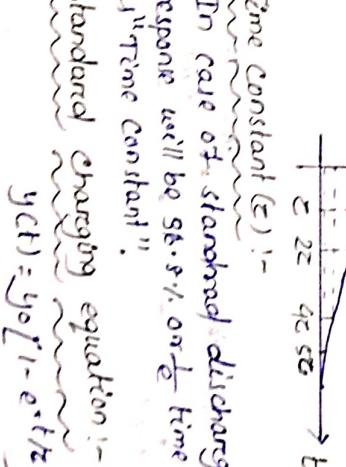Time constant τ :- In case of standard charging equation, the time at which response will be 63.3% of its initial value is referred as "time constant".




Time Constant (τ) :-

In case of standard discharging equation, the time at which response will be 63.3% of its initial value is referred as "time constant".

Standard charging equation :-

$$y(t) = y_0 [1 - e^{-t/\tau}]$$

where τ = Time Constant

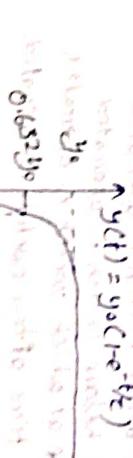

Time constant

In case of standard charging equation, the time at which response will be 63.3% of its initial value is referred as "time constant".

Generalized equation of both charging and discharging:

$$(y(t)) = y(\infty) + [y(0) - y(\infty)] e^{-\frac{t}{\tau}}$$

This eqn valid only for first order differential eqn.


$$\boxed{\frac{dy(t)}{dt} + \frac{1}{\tau} y(t) = c}$$

where, $c = \text{rhs}$



switching [$t=0$]

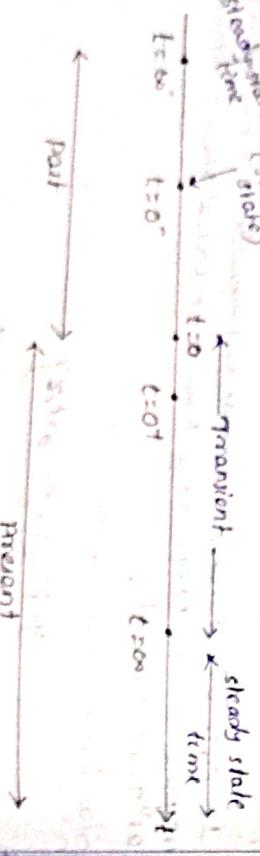Because of fast transition time
current through inductor can't change (it can't flow)
one node is dc means
second cannot



- (i) $t=0^+$ represents momentum time after switch is operated.
- (ii) $t=0^+$ represents transition time before switch is operated.
- (iii) $t=0^-$ represents steady-state time before switch is operated.
- (iv) $t=0^+$ represents steady-state time before switch is operated.

After operated, if $t=0 \rightarrow$ steady state (Present)

or $t=0 \rightarrow$ steady state (Past)

Transient Behaviour of Inductor

Law of Inductance



$$V_L(t) = L \frac{dI}{dt} \quad [\text{Ohm's law}]$$

$$I(t) = \frac{1}{L} \int_0^t V_L(t') dt \quad [\text{Kho's law}]$$

$$V_L(t) = I(t) + \frac{1}{L} \int_0^t V_L(t') dt$$

memory element

$I(0^+) = \text{Initial current of Inductor}$

$E(0^+) = \frac{1}{2} (I(0^+))^2 \text{ Joule}$

$I(0^-) = \text{Initial Energy of Inductor}$

Property of Inductor:-

It opposes the change of current

$$\boxed{I(0^+) = I(0^-)}$$

It opposes the change of energy

$$\boxed{E(0^+) = E(0^-)}$$



It allows sudden change in voltage

$$V(0^+) \neq V(0^-)$$

It opposes the change in flux

$$\text{Inductor: } \boxed{V(0^+) = V(0^-)}$$

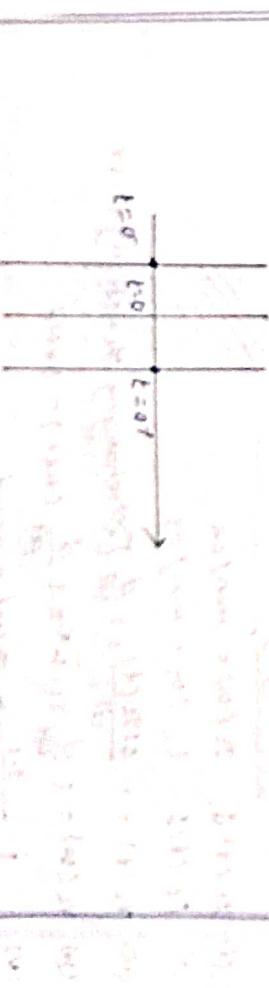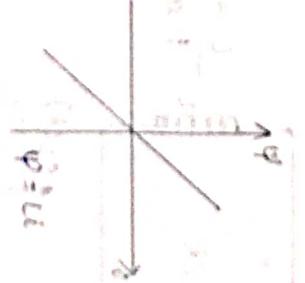In Inductor, from $t=0$ to $t=0^+$, current & energy are same.



⇒ Steady-state behaviour of induction

Care -1


- (v) $\text{Tr}(t) \uparrow$ $\text{Tr}(\infty) = \text{maximum}$
 $E_t(t) \uparrow$ $E_t(\infty) = \text{maximum}$

(vi) $V_t(t) = t \frac{d\text{Tr}(t)}{dt} = t \frac{d}{dt} [\text{Increasing function}] = \text{true value}$

(vii) $V_t(\infty) = t \frac{d\text{Tr}(\infty)}{dt} = t \frac{d}{dt} [\text{maxm value}] = \text{overvolt}$

(viii) $L & \text{Inductance} \xrightarrow{\text{series}} \text{S.C. [short circuit]}$

steady-state condition

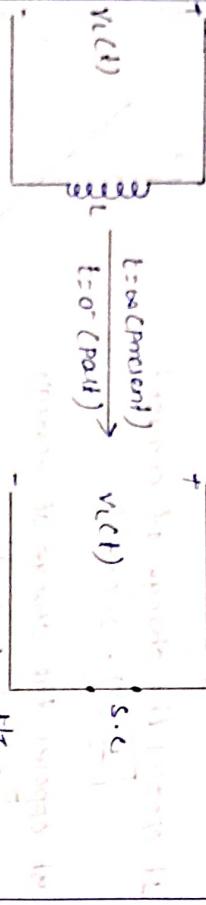

The figure consists of two graphs sharing a common vertical axis labeled $V_L(t)$.

Graph 1 (Top): Shows the inductor voltage $V_L(t)$ versus time t . The curve starts at zero and increases exponentially towards a steady-state value labeled $V_{L(\infty)}$. A horizontal dashed line represents the steady state. An arrow points from the label "charging of inductor" to the curve.

Graph 2 (Bottom): Shows the inductor voltage $V_L(t)$ versus time t . The curve starts at a positive value labeled $V_{L(0)}$ and decreases exponentially towards zero. An arrow points from the label "V_L(0) = Overall initial voltage" to the curve.

Case-3
Discharging of Inductor:-

$$(ii) \quad x_L(t) \downarrow \quad \pi_L(\infty) = \min_{t \geq 0} \pi_t$$

$$(iii) \quad E_L(t) \downarrow \quad E_L(\infty) = \min f_{\text{opt}}$$

$$(iv) \quad n(\omega) = 1 \frac{d}{dt} N(\omega) = 1 \frac{d}{dt} (m$$

$L \xrightarrow{\text{S.S.}}$ short circuit

Transient Behaviour of Capacitor

$$= \frac{1}{2} \left(\frac{\partial^2 \tilde{w}}{\partial x^2} + \frac{\partial^2 \tilde{w}}{\partial y^2} \right)$$

Capacitor

$$\frac{dy}{dx} = ?$$

$$q(t) = c \cdot r(t)$$

A graph with a horizontal axis labeled V and a vertical axis labeled I . A straight line with a negative slope passes through the origin, representing Ohm's law for a resistor.

$$W(t) = \frac{1}{t} \int_0^t \omega(s) ds$$

$$v(t) = \frac{1}{C} \int_0^t x(t) dt + \frac{1}{C} \int_0^t u(t) dt$$

$$V_C(0^+) = \text{initial voltage at capacitor} \\ E_C(0^+) = \frac{1}{2} C V_C(0^+)^2 \text{ Joule} \quad [\text{Initial energy}]$$

Reportedly of character 1

Property of capacitor :-
 It opposes change of voltage i.e. $V_c(t) = V_c(0)$ ->
 It opposes change of charge i.e. $q_c(t) = q_c(0)$ ->
 It opposes change of energy i.e. $E_c(t) = E_c(0)$ ->

- gt opposes at change of voltage i.e $V(t) = V_0 e^{-t/\tau}$
- gt oppose at change of charge i.e $q(t) = q_0 e^{-t/\tau}$
- gt opposes at change of energy i.e $E(t) = E_0 e^{-t/\tau}$


$\tau_C = \frac{1}{\omega} \ln 2$

gt allows sudden change in current i.e $I(t) \neq I_0 e^{-t/\tau}$

Steady-state behaviour of capacitor

Condition (i) $\nabla f(x) \rightarrow$ Increase $\Rightarrow \nabla f(\infty) = \text{maximum}$

$$(iv) I_C(\infty) = C \frac{dV_C(\infty)}{dt} = C \frac{d}{dt}(0) = 0 \quad [\text{open circuit}]$$

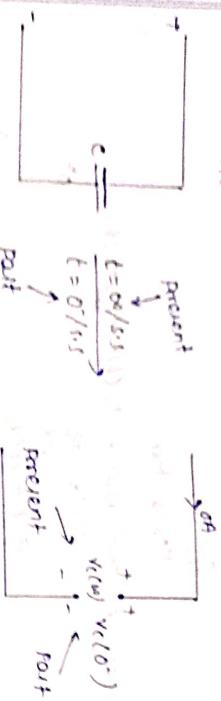


Case 2

(i) $V_C(t) \rightarrow$ zero mean \downarrow $V_C(0) = \text{minimum}/0.4V$


(ii) $E_C(t) \rightarrow$ zero mean \downarrow $E_C(0) = \text{min } 0.16J$

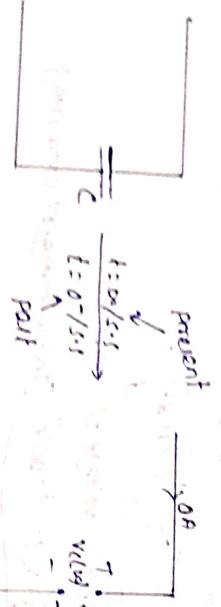(iii) $I_C(t) = C \frac{dV_C(t)}{dt} = -i_R$

$$(iv) I_C(\infty) = C \frac{dV_C(\infty)}{dt} = C \frac{d}{dt}(0) = 0 \quad [\text{open circuit}]$$



AC Response of an R-C Circuit

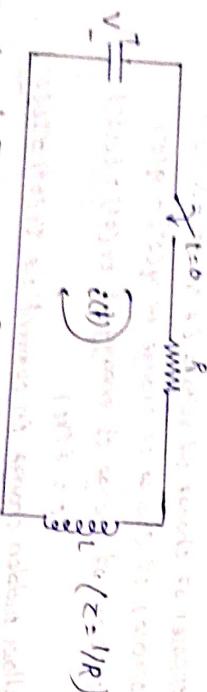

Generalized Transient eqn

$$i(t) = i(0+) + [i(0+) - i(\infty)] e^{-Rt/L}$$

$$i(0+) = i(0-) = 0A$$

$$i(\infty) = \frac{V}{R}$$

$$i(t) = \frac{V}{R} + \left[0 - \frac{V}{R} \right] e^{-Rt/L}$$

$t = 0^+$

$$i(t) = \frac{V}{R} [1 - e^{-Rt/L}] \rightarrow \text{charging eqn}$$

Inductor voltage $V_L(t)$

$$V_L = L \frac{di}{dt}$$


$$V_L = L \frac{d}{dt} \left(\frac{V}{R} - \frac{V}{R} e^{-Rt/L} \right)$$

$$V_L = \frac{VR}{R} (0 + \frac{R}{L} e^{-Rt/L})$$

$$V_L = V_0 e^{-Rt/L}$$

\rightarrow discharging exp

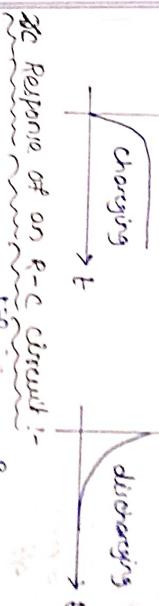$i(t) \uparrow$ charging
 $i(t) \downarrow$ discharging




Generalized Transient eqn

$$V_C(t) = V_C(\infty) + [V_C(0+) - V_C(\infty)] e^{-Rt/C}; t > 0$$

$$\Rightarrow V_C(t) = V_C(0+) = 0V$$

$$\Rightarrow C = R_{THC} \text{ see.}$$


Generalized Transient eqn

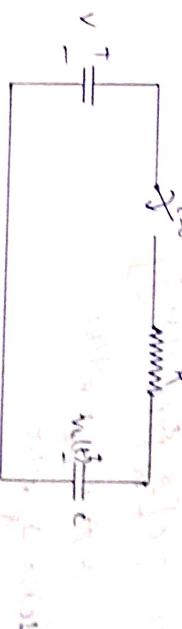

$$i_C(t)$$

$$V$$

$$i_C(t) = i_C(0+) e^{-Rt/C}$$

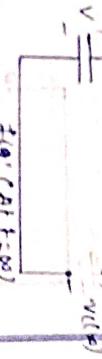

$$i_C(t) = i_C(0+) e^{-Rt/C}$$

$t = 0^+$

2 in 1

$$\underline{UVL} = V + \Sigma c(C_0^+) R + o \geq 0$$

$$\Rightarrow \tau_C(\varrho_f) =$$

$$v_c(t) = v_c(\infty) + [v_c(0^+) - v_c(\infty)] e^{-t/\tau} \quad ; \quad t > 0$$

$$2f_1 - \alpha [V - 0] + V = f_2 V$$

$$V_C(t) = V \left[1 - e^{-t/\tau_C} \right]$$

$$\rightarrow Tc(t) = Tc(\infty) + [Tc(0^+) - Tc(\infty)] e^{-t/\tau} ; t \gg 0$$

$$T_{\text{eff}} = 0 + \left[\frac{\lambda}{\sigma} - \sigma \right] \cdot \frac{1}{2} \cdot \ln \left(\frac{L}{M} \right) = 1710$$

$$f(x) = \frac{N}{x} e^{-x/2}; x \geq 0$$

$$w(\tau, t) = \frac{C}{\sqrt{\tau - t}}$$


$$= C \left[\frac{d}{dt} \int_{\Omega} U(1 - e^{-t/\tau}) \right]$$

$$f(x) = \frac{1}{\sqrt{2\pi}} e^{-x^2/2}$$

卷之三

The response of an RLC series circuit

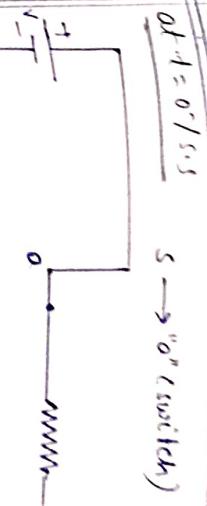1. $\text{H}_2\text{O} + \text{NaCl} \rightarrow \text{H}_2\text{O} + \text{NaCl}$



$$f_1(0^\circ) = c(0^\circ) = DA$$

Applied NLP for NLP

二十一

$$\Rightarrow \text{vol} = \text{volt}$$

$$\overline{of t=0} \rightarrow a \text{ to } b$$

$$\Rightarrow \pi_C(0+) = \pi_C(0-) \quad [\pi_C(t) = \pi_C(t+)]$$

$$\Rightarrow V_C(0+) = V_C(0-) = V_{\text{volt}}$$

$$\frac{\partial f}{\partial t} = 0$$

$$\downarrow S_L(D^+) = D_F$$

— 14 —

$$W_1 \rightarrow \overline{W_1} + W_2 + W_3$$