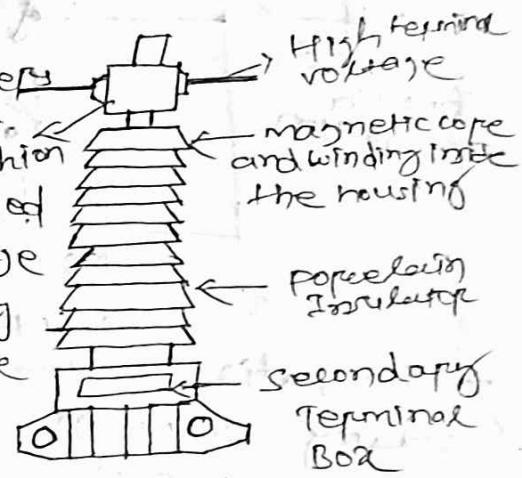


current transformer (CT) !-

- Def'n - A current transformer is a device that is used for the transformation of current from a high value into a proportionate current to lower value.
- It transforms the high voltage current into the high voltage current into the low voltage current due to which the heavy currents flows through the transmission lines is safely monitored by the ammeter.
- The current transformer is used with the AC instrument, meters or control apparatus where the current to be measured is of such magnitude that the meter or instrument core cannot conveniently be made of sufficient current carrying capacity.
- The current transformer is shown in the Fig. below.
- The primary and secondary current of the current transformer are proportional to each other.
- The current transformer is used for measuring the high ~~high~~ voltage current because of the difficulty of inadequate insulation in the meter itself.
- The current transformer is used for meters for measuring the current up to 100 amperes.



construction of current Transformers:-

- The core of the current transformer is built up with lamination of silicon steel for getting a high degree of accuracy the permalloy or numental is used for the yoking cores.
- The primary windings of the current transformer carry the current which is to be measured, and it is connected to the main ckt.
- The transformer carries the current which


to be measured, and this is connected to the main ckt.

→ The secondary windings of the transformer can be connected to the current to be measured, and it is connected to the current in the power ckt.

→ In a current transformer, the load's impedance or burden on the secondary windings of the meter or the instruments, measured, and the primary and the secondary windings are connected to each other.

→ The primary winding is a single turn winding located across the cores and carries the full load current.

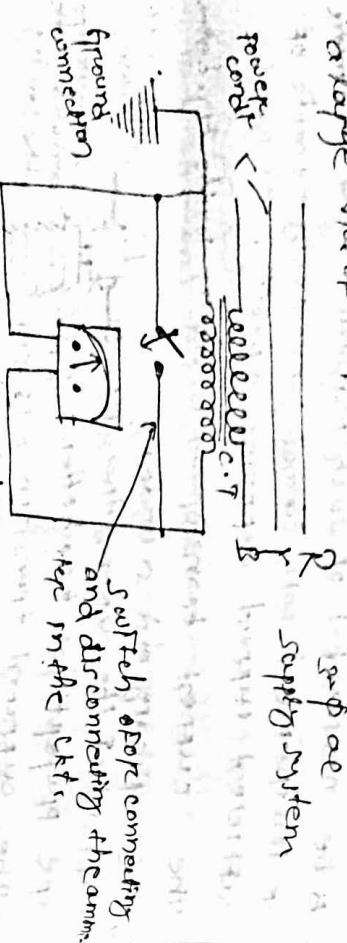→ The secondary winding of the transformer has a large no. of turns.



(0-5A Ammeter)

→ The ratio of the primary current and the secondary current is known as current transformer ratio of the ckt.

→ The current ratio of the transformer is usually

high.

→ The secondary current ratings are of the order of 5A, 1A and 0.1A.

→ The current primary ratings vary from 10A to 3000A or more.

→ The symbolic representation of the current transformer is shown in the Figure below.

→ The primary voltage induced in the primary winding of the transformer is proportional to the number of turns and the flux density in the core.

→ The working principle of the current transformer is slightly different from that of a power transformer.

→ In a current transformer, the load's impedance or burden on the secondary winding has nothing differed from the power transformers.

→ Thus, the current transformer operates on secondary ckt conditions.

Phasor Diagram of Current Transformer:

→ The phasor diagram of the current transformer is shown in the figure below.

→ The main flux is taken as a reference. The primary and secondary induced voltages are lagging behind the main flux by 90° .

→ The magnitude of the primary and secondary voltages depends on the no. of turns on the winding.

→ The excitation current induces by the component of magnetising and working current.

where, I_s = secondary current

E_s = secondary induced voltage

I_p = primary current.


E_p = primary induced voltage

K_t = turn ratio, no. of secondary turns/ no. of turns of primary

I_{ex} = excitation current.

I_m = magnetising component

I_w = main flux

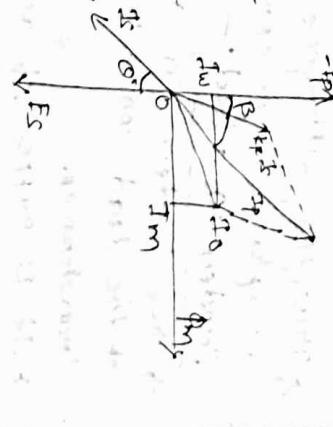

→ The secondary current lags behind the primary current by an angle θ .

→ The secondary induced voltage is proportional to the primary current. The secondary current relocates to the primary side by reversing the secondary current and multiplying by the turn ratio.

→ The currents flow through the primary & the sum of the existing current & the primary current, I_1 , is the total primary current.

→ The current transformer has two errors - ratio and phase angle errors.

→ The current transformer has two errors - ratio & phase angle errors.

Current Ratio Errors:

The current transformer is mainly due to the energy component of excitation current and is given as, Ratio Error = $\frac{I_2}{k_1 I_1} - 1$.

Where I_2 is the primary current, k_1 is the turns ratio and I_1 is the secondary current.

Phase Angle Error: - In an ideal current transformer the vector angle between the primary and

reversed secondary current is zero.

But in an actual current transformer, there is a phase difference between the primary and the secondary current because the primary current has also supplied the component of existing current as a phase angle error.

Burden on a load: - The burden of a current transformer is the value of the load connected across the secondary of the load connected across the secondary of the transformer.

It is expressed as the output in volt amperes.

The rated burden is the value of the burden on the nameplate of the CT.

The rated burden is the product of the ratio and current on the secondary when the CT carries the rated value of current.

It suppresses the instrument or relay with its

rated value of current.

Application of current transformers:-

→ These transformers are used to measure entire power in power houses, industries, and stations, conference rooms, in industries for meeting relaying of analog the flow of current in the circuit also for protection purposes.

Potential Transformer (PT) :-

→ The potential transformer may be defined as an instrument transformer used for the transformation of voltage from a higher value to lower value.

→ This transformer stepdown the voltage to a safe limit value which can be easily measured by the ordinary low voltage instrument like a voltmeter, wattmeter and watt-hour meters, etc.

Construction of Potential Transformer:-

→ The PT is made with high-quality core operating at low flux density so that the magnetizing current is small.

→ The terminal of the transformer should be designed so that the variation of the voltage ratio with load is minimum and the phase shift b/w the input and output voltage is also minimum.

→ The primary winding has a large no. of turns, and the secondary winding has a much smaller no. of turns.

→ For reducing the leakage reactance, the windings are used in the potential transformer.

→ The insulation cost is also reduced by dividing the primary winding into the sections which reduce the insulation b/w the layers.


Connection of Potential Transformer:-

→ The PT is connected in parallel with the CT.

→ The primary windings of the PT are directly connected to the powerckt whose voltage is to be measured.

→ The secondary terminals of the PT are connected to the measuring instrument like the voltmeter, wattmeter etc.

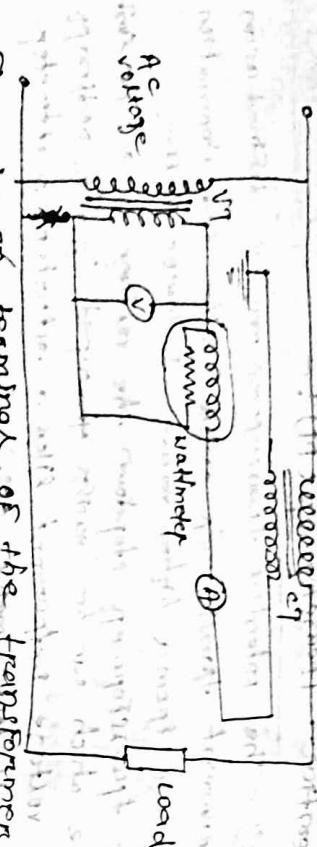→ The secondary windings of the potential transformer are magnetically coupled through the magnetic core of the primary windings.



- The primary terminal of the transformer is rated for several thousand volts, and the secondary terminal is always rated below 100V.
- The ratio of the primary voltage to the secondary voltage is referred as transformation ratio or turns ratio.
- Ratio and phase angle errors of potential transformer

- In an ideal PT, the primary and the secondary voltage is exactly proportional to their primary voltage and exactly in phase opposition.

- But this cannot be achieved practically due to the primary and secondary voltage drops.

Thus, both the primary and secondary voltage is.

introduced in the system.

voltage ratio error = The voltage ratio error

is expressed in regarding measured voltage, and

it is given by the formula

$$\text{Ratio error} = \frac{k_p - k_{no-load}}{k_p}$$

where, k_p is the nominal ratio, i.e. the ratio of the rated primary voltage and the rated secondary voltage.

Phase Angle Error:— The phase angle error is the error between the secondary terminal voltage which is exactly in phase opposition with the primary terminal voltage.

→ The increase in the no. of instruments in the relay connected to the secondary of the PT will increase the errors in the potential transformers.

Burden of a Potential Transformer:

- The burden is the total external volt-amp loading.
- The secondary at rated secondary voltage is the limiting or maximum burden is greatest at the rated burden of a PT is a VA burden which must not be exceeded if the transformer is to operate with its rated capacity.
- The rated burden is indicated on the name plate.
- The primary induced emf is limited by the load on which the PT will operate continuously without overheating its winding beyond the permissible limits.
- This burden is several times greater than the rated burden.

Phasor Diagram of a Potential Transformer

→ The phasor diagram of the potential transformer is shown in Fig.

where, I_s = secondary induced current

E_s = secondary induced emf

V_s = secondary terminal voltage

R_s = secondary winding resistance

X_s = secondary winding reactance

I_p = primary current

E_p = primary induced emf

V_p = primary terminal voltage

R_p = primary winding resistance

X_p = primary winding reactance

$I_{no-load}$

I_s

I_p

E_p

V_p

R_p

X_p

E_s

V_s

R_s

X_s

I_s

I_p

$I_{no-load}$

E_p

V_p

R_p

X_p

E_s

V_s

I_s

I_p

$I_{no-load}$

E_p

V_p

R_p

X_p

E_s

V_s

I_s

I_p

$I_{no-load}$

E_p

V_p

R_p

X_p

E_s

V_s

I_s

I_p

$I_{no-load}$

E_p

V_p

R_p

X_p

E_s

V_s

I_s

I_p

$I_{no-load}$

E_p

V_p

R_p

X_p

E_s

x_p = primary winding reactance.

k_p = Turn Ratio

I_0 = excitation current

I_m = magnetising component of I_0

I_w = core loss component of I_0

ϕ_m = main flux in number of turns.

θ = phase angle error.

→ the main flux is taken as a reference. In the instrument transformer, the primary current is the vector sum of the excitation current I_0 and the current equal to the reversal secondary current.

It is multiplied by the ratio of $1/k_p$.

→ The v_p is the voltage applied to the primary terminal of the PT.

→ The voltage drop due to resistance and reactance of primary winding due to primary current is given by $i_p x_p$ and $i_p r_p$.

→ When the voltage drop subtracts from the primary voltage of the PT, the primary induced emf will appear across the terminals.

→ This primary emf of the transformer will transform into secondary winding by mutual induction and converted into secondary induced emfs.

→ This emf will drop by the secondary winding resistance and reactance, and the resultant voltage will appear across the secondary terminal voltage, and it is denoted by v_s .

Applications of PT:

→ It is used for metering purpose.

→ For the protection of the feeders.

→ For protecting the impedance of the generators.

→ For synchronising the generators and feeders.